

### Inverter:

Inverter is a power electronic circuit which converts dc signal into ac signal of a specific frequency. The output of inverter could be single-phase ac or three-phase ac, but it is not possible to obtain a pure sinusoidal ac voltages from the practical inverters. The various applications of inverters are battery back up, ac supply, variable frequency ac motor drives, etc.


### Single-phase Inverters:

Let,  $f_0$  = Required frequency of ac voltage.


Then, time period of ac output voltage  $T = \frac{1}{f_0}$ .

For first  $\frac{T}{2}$ ,  $S_1$  is turned on keeping  $S_2$  off. The output follows the path
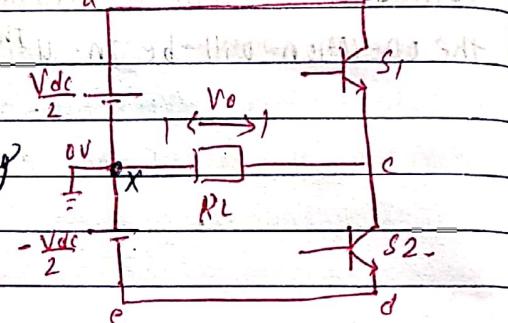
$$a - b - S_1 - c - R_L - x \text{ i.e., } V_o = i_o R_L$$



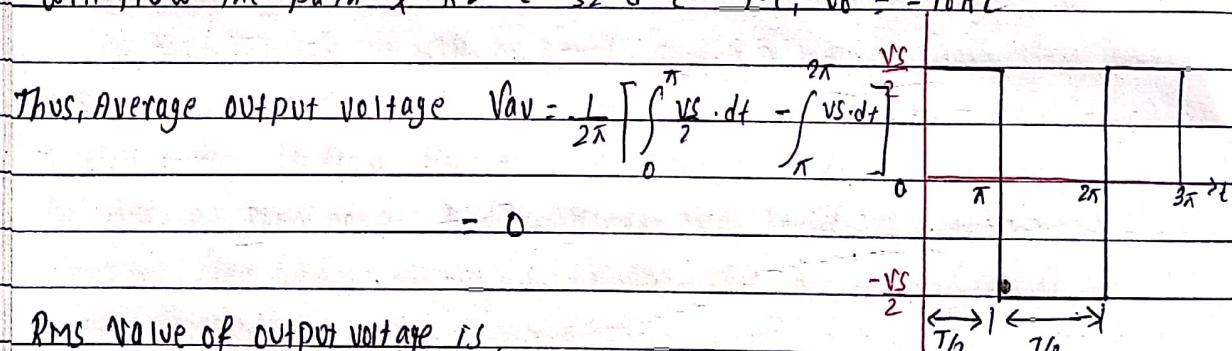For another  $\frac{T}{2}$ ,  $S_2$  is turned on keeping  $S_1$  off. Then current will flow the path  $x - R_L - c - S_2 - d - e$  i.e.,  $V_o = -i_o R_L$



RMS value of output voltage is,

$$V_{rms} = \left[ \frac{1}{2\pi} \int_0^{\frac{\pi}{2}} \left( \frac{V_o}{2} \right)^2 dt + \int_{\frac{\pi}{2}}^{2\pi} \left( -\frac{V_o}{2} \right)^2 dt \right]^{1/2}$$

$$= \left[ \frac{1}{2\pi} \left( \frac{V_o}{2} \right)^2 \int_0^{\pi} dt + \int_{\pi}^{2\pi} \left( \frac{V_o}{2} \right)^2 dt \right]^{1/2}$$

$$= \sqrt{\frac{1}{2\pi} \times \left( \frac{V_o}{2} \right)^2 \times 2\pi}$$

$$= \frac{V_o}{2}$$

Fourier Analysis:

$$V_0 = \frac{A_0}{2} + \sum_{n=1}^{\infty} (A_n \cos n\omega t + B_n \sin n\omega t)$$

$$\begin{aligned} A_0 &= \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{V_s}{2}\right) d\omega t + \int_{\pi}^{2\pi} \left(-\frac{V_s}{2}\right) d\omega t \right] \\ &= \frac{1}{\pi} \left[ \left(\frac{V_s}{2}\right) (\pi - 0) - (\pi - 2\pi) \right] = \frac{V_s}{2\pi} [\pi - \pi] = 0 \end{aligned}$$

$$A_n = \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{V_s}{2}\right) \cos n\omega t d\omega t + \int_{\pi}^{2\pi} \left(-\frac{V_s}{2}\right) \cos n\omega t d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ \int_0^{\pi} \cos n\omega t d\omega t - \int_{\pi}^{2\pi} \cos n\omega t d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ \frac{\sin n\omega t}{n} \Big|_0^{\pi} - \frac{\sin n\omega t}{n} \Big|_{\pi}^{2\pi} \right] = 0$$

$$B_n = \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{V_s}{2}\right) \sin n\omega t d\omega t + \int_{\pi}^{2\pi} \left(-\frac{V_s}{2}\right) \sin n\omega t d\omega t \right]$$

$$= \frac{2}{2\pi} \left(\frac{V_s}{2}\right) \left[ \int_0^{\pi} \sin n\omega t d\omega t - \int_{\pi}^{2\pi} \sin n\omega t d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ -\frac{\cos n\omega t}{n} \Big|_0^{\pi} + \frac{\cos n\omega t}{n} \Big|_{\pi}^{2\pi} \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ 1 - \cos n\pi + \cos 2n\pi - \cos n\pi \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ 1 - 2\cos n\pi + \cos 2n\pi \right]$$

$$= \frac{1}{\pi} \left(\frac{V_s}{2}\right) \left[ 1 - 2 \cdot (-1)^n + 1 \right]$$

$$= \frac{1}{n\pi} \left( \frac{VS}{2} \right) [ 2 - 2(-1)^n ]$$

For n = odd

$$= \frac{VS}{2\pi n} [ 2 - 2(-1)^n ] = \frac{VS}{2\pi n} [ 2 - 2 \times 1 ]$$

$$= \frac{VS}{\pi n} [ 1 - (-1)^n ] = 0$$

$$\text{Then, } B_1 = \frac{VS}{\pi \cdot 1} [ 1 - (-1)^1 ] \Rightarrow 2 \frac{VS}{\pi} = \left( \frac{VS}{2} \right) \cdot \frac{4}{\pi} = 1.2732 \left( \frac{VS}{2} \right)$$

$$B_3 = \frac{VS}{3\pi} [ 1 - (-1)^3 ] = \frac{2 VS}{3\pi} = \left( \frac{VS}{2} \right) \cdot \frac{4}{3\pi} = 0.4244 \left( \frac{VS}{2} \right)$$

$$B_5 = \frac{2 VS}{5\pi} = \left( \frac{VS}{2} \right) \cdot \frac{4}{5\pi} = 0.2546 \left( \frac{VS}{2} \right)$$

Now,

$$V_0 = \frac{A_0}{2} + \sum_{n=1}^{\infty} A_n \cos n\omega t + B_n \sin n\omega t.$$

$$= \sum_{n=1, 3, 5, 7, \dots}^{\infty} \frac{VS}{\pi n} [ 1 - (-1)^n ] \sin n\omega t.$$

$$= 2 \frac{VS}{\pi} \sin \omega t + \frac{2}{3} \frac{VS}{\pi} \sin 3\omega t + \frac{2}{5} \frac{VS}{\pi} \sin 5\omega t + \dots$$

$$1.2732 \left( \frac{VS}{2} \right)$$

$$0.4244 \left( \frac{VS}{2} \right)$$

$$0.2546 \left( \frac{VS}{2} \right)$$

$$0.0231 - 0.0231 - 0.0231 - 0.0231 - 0.0231 - 0.0231$$



Single phase inverter with AC motor load.

In order to make mathematical analysis of this circuit simpler, let us make an assumption that sinusoidal back emf of ac motor ( $e_0$ ) is in synchronism with inverter switching frequency and is purely sine wave without any harmonics.

Let, inverter frequency  $f_p = 1$  Hz.

$$\therefore \omega_0 = 2\pi f_0 \text{ rad/sec.}$$
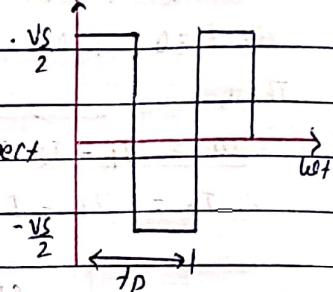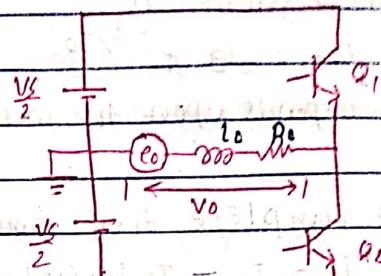
$$e_0 = E_0 \sin(\omega t + \epsilon_0), \quad \epsilon_0 = \text{angle of lead with respect to O/P voltage.}$$



For positive half cycle.

$$\frac{V_s}{2} = E_0 \sin(\omega t + \epsilon_0) + R_0 i_0 + L_0 \frac{di_0}{dt}.$$

The solution of this equation has three parts.

i)  $i_{01}$  = A steady state part associated with driving function  $\frac{V_s}{2}$  and is given by

$$i_{01} = \frac{V_s}{2R_0} = I_1$$

ii)  $i_{02}$  = A steady state part associated with driving function  $E_0 \sin(\omega t + \epsilon_0)$  and is given by:

$$i_{02} = \frac{E_0}{R_0 + j\omega_0 L_0} \sin(\omega t + \epsilon_0 - \delta_0) \quad \text{where, } \delta_0 = \tan^{-1} \left( \frac{\omega_0 L_0}{R_0} \right)$$

$$i_{02} = \frac{E_0}{|Z_0|} \sin(\omega t + \epsilon_0 - \delta_0) \quad \text{where, } |Z_0| = \sqrt{R_0^2 + (\omega_0 L_0)^2}$$

$$i_{02} = I_2 \sin(\omega t + \epsilon_0 - \delta_0) \quad \text{where, } I_2 = \frac{E_0}{Z_0}$$

iii)  $i_{03}$  = Transient part is given by solution of the following equation.

$$L_0 \frac{di_{03}}{dt} + R_0 i_{03} = 0$$

whose solution is

$$i_{03} = I_3 e^{-t/T_0} \quad \text{where, } T_0 = \frac{L_0}{R_0} = \text{time constant.}$$

$I_3$  depends upon the initial condition of the circuit.

The complete time domain solution is

$$i_0 = I_1 - I_2 \sin(\omega t + \phi_0 - \delta_0) + I_3 e^{-t/T_0}$$

$I_3$  can be calculated by setting initial condition as,

At  $t=0$ ,  $i_0 = I_a$  (may be zero also)

Then,

$$I_a = I_1 - I_2 \sin(\phi_0 - \delta_0) + I_3 e^{0/T_0} = I_1 - I_2 \sin(\phi_0 - \delta_0) + I_3$$

$$\therefore I_3 = I_a - I_1 + I_2 \sin(\phi_0 - \delta_0)$$

At the end of 1<sup>st</sup> half cycle, at  $\theta = \pi$ , let

$\omega t = \pi$ ,  $i_0 = I_b$ , then.

$$I_b = I_1 - I_2 \sin(\pi + \phi_0 - \delta_0) + I_3 e^{-\pi/T_0}$$


The solution of -ve half cycle is given by

$$i_0 = -I_1 - I_2 \sin(\theta + \phi_0 - \delta_0) + I_4 e^{-\theta/T_0}$$

To calculate  $I_4$  at  $\theta = \pi$ ,  $i_0 = I_b$ .

$$I_4 = I_b + I_1 + I_2 \sin(\pi + \phi_0 - \delta_0)$$

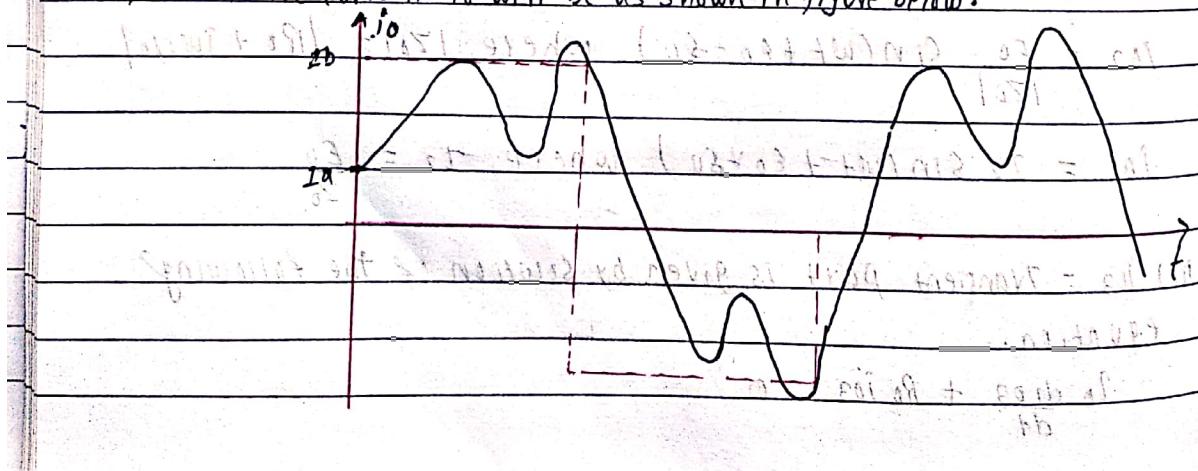Following this procedure we can step through successive half cycle and determine two cycle circuit response to any initial condition  $i_0$ . The waveform of load current  $i_0$  will be as shown in figure below.



### Three phase Inverter:

Basically a three phase inverter is the combination of three sets of single phase inverters supplied from a common dc source and each set conducted with a phase difference of  $120^\circ$  to each other.

Let, 'O' is the mid-point of

dc supply which is

Considered as reference  $\frac{V_S}{2}$


Potential point for

evaluating the

Potential of various

points of the circuit.

$-\frac{V_S}{2}$

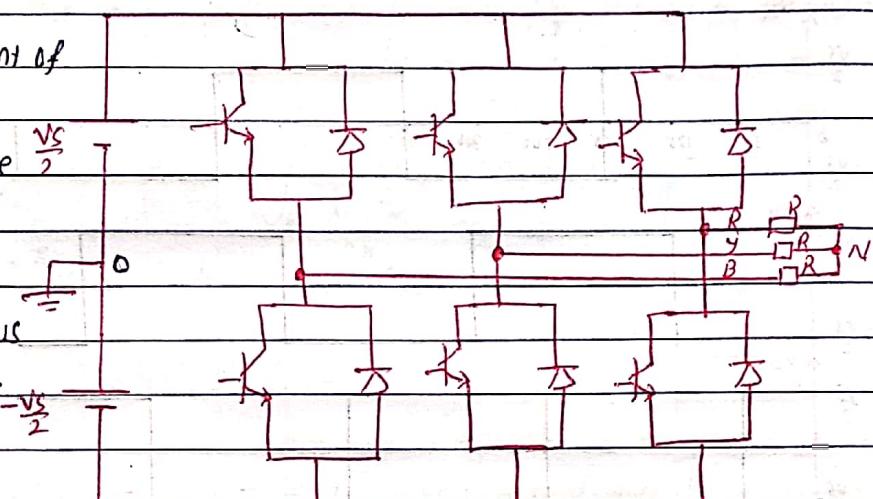

Let,  $V_R$  = Potential of R phase terminal w.r.t 'O'

$V_Y$  = Potential of Y phase terminal w.r.t 'O'.

$V_B$  = Potential of B phase terminal w.r.t 'O'.

The voltage between o/p terminals are given by

$$V_{RY} = V_R - V_Y$$

$$V_{YB} = V_Y - V_B$$

$$V_{BR} = V_B - V_R$$

Considering 3-phase balanced load.

$$V_{RN} + V_{YN} + V_{BN} = 0$$

$$\text{And, } V_{RN} = V_R - V_N \Rightarrow V_R = V_{RN} + V_N.$$

$$V_{YN} = V_Y - V_N \Rightarrow V_Y = V_{YN} + V_N.$$


$$V_{BN} = V_B - V_N \Rightarrow V_B = V_{BN} + V_N.$$

$$\text{Then, } V_R + V_Y + V_B = 3V_N + (V_{RN} + V_{YN} + V_{BN})$$

$$\therefore V_N = \frac{1}{3} (V_R + V_Y + V_B)$$

Now, the phase voltage is given by  $V_{RN} = V_R - V_N$ .

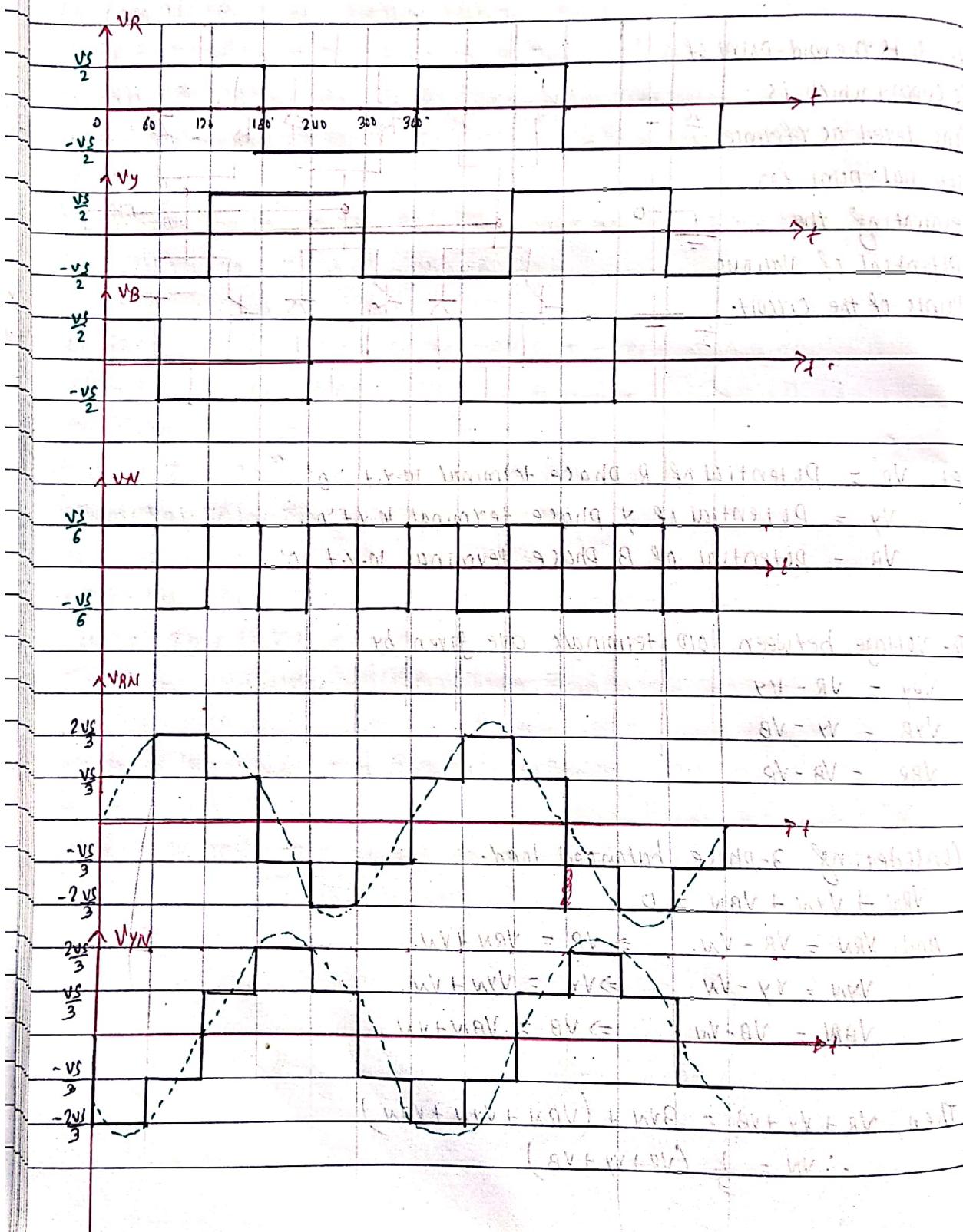
Similarly, the  $V_{YN}$  and  $V_{BN}$  will be similar to that of  $V_{RN}$ , but with  $120^\circ$  out of phase with each other. It is clear from the waveform that frequency of  $V_N$  is 3 times greater than that of frequency of  $V_R$ .



Fourier analysis of three phase inverters.

The wave form of VR is as shown in figure below.
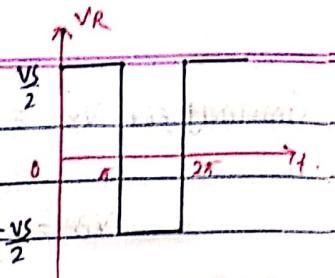
$$V_o(t) = \frac{A_0}{2} + \sum_{n=1}^{\infty} (A_n \cos n\omega t + B_n \sin n\omega t)$$



$$A_0 = \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{vs}{2}\right) d\omega t + \int_{\pi}^{2\pi} \left(-\frac{vs}{2}\right) d\omega t \right] = \frac{1}{\pi} \left(\frac{vs}{2}\right) [(0-\pi) - (2\pi-\pi)] \\ = 0$$

$$A_n = \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{vs}{2}\right) \cos n\omega t \cdot d\omega t + \int_{\pi}^{2\pi} \left(-\frac{vs}{2}\right) \cos n\omega t \cdot d\omega t \right] \\ = \frac{2}{2\pi} \cdot \left(\frac{vs}{2}\right) \left[ \int_0^{\pi} \cos n\omega t \cdot d\omega t - \int_{\pi}^{2\pi} \cos n\omega t \cdot d\omega t \right]$$

$$= 0$$

$$B_n = \frac{2}{2\pi} \left[ \int_0^{\pi} \left(\frac{vs}{2}\right) \sin n\omega t \cdot d\omega t + \int_{\pi}^{2\pi} \left(-\frac{vs}{2}\right) \sin n\omega t \cdot d\omega t \right] \\ = \frac{2}{2\pi} \left(\frac{vs}{2}\right) \left[ -\frac{\cos n\omega t}{n} \Big|_0^{\pi} + \frac{\cos n\omega t}{n} \Big|_{\pi}^{2\pi} \right] \\ = \frac{1}{n\pi} \left(\frac{vs}{2}\right) [1 - \cos n\pi + \cos 2n\pi - \cos n\pi] \\ = \frac{1}{n\pi} \left(\frac{vs}{2}\right) [1 + 1 - 2 \cdot (-1)^n] \\ = \frac{1}{n\pi} \left(\frac{vs}{2}\right) \cdot 2 [1 - (-1)^n]$$

For,  $n = \text{even}$

$$B_n = 0$$

For  $n = \text{odd}$ .

$$B_n = -\frac{1}{n\pi} \left(\frac{vs}{2}\right) \cdot 2 \cdot 2 \Rightarrow \frac{4}{n\pi} \left(\frac{vs}{2}\right)$$

$$\text{Then, } V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4}{n\pi} \left(\frac{vs}{2}\right) \sin n\omega t$$

$$= \frac{4}{\pi} \left(\frac{vs}{2}\right) \sum_{n=1,3,5}^{\infty} \frac{1}{n} \sin n\omega t$$

Similarly for  $V_y = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{2\pi}{3})]$

$V_B = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{4\pi}{3})]$

We can break these series in three sub-series as follows.

$n = 1, 7, 13, \dots \quad 3, 9, 15, \dots \quad 5, 11, 17, \dots$

So that,

In 1<sup>st</sup> sub-series we get 1<sup>st</sup>, 7<sup>th</sup>, 13<sup>th</sup>, ... harmonics and so on.

In 2<sup>nd</sup> sub-series we get 3<sup>rd</sup>, 9<sup>th</sup>, 15<sup>th</sup>, ... harmonics and so on.

In 3<sup>rd</sup> sub-series we get 5<sup>th</sup>, 11<sup>th</sup>, 17<sup>th</sup>, ... harmonics and so on.

For the 1<sup>st</sup> sub-series,  $n = 1, 7, 13, \dots$

$n = (1+6K), K = 0 \text{ to } \infty$

$V_R = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=1,7,13,\dots}^{\infty} \frac{1}{n} \sin[nwt]$

$V_y = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=1,7,13,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{2\pi}{3})]$

$V_B = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=5,11,17,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{4\pi}{3})]$

The first sub-series represents Positive sequence system voltage.

For the 2<sup>nd</sup> sub-series,  $n = 3, 9, 15 = 3+6K$  Where,  $K = 0 \text{ to } \infty$ .

$V_R = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=3,9,15,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{2\pi}{3})]$

$V_y = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=3,9,15,\dots}^{\infty} \frac{1}{n} \sin[n(wt)]$

$V_B = \frac{U}{\pi} \left(\frac{V_s}{2}\right) \sum_{n=3,9,15,\dots}^{\infty} \frac{1}{n} \sin[n(wt - \frac{4\pi}{3})]$

$$\begin{aligned} \text{Now, } \sin[n(wt - \frac{2\pi}{3})] &= \sin[nwt - (3+6k)\frac{2\pi}{3}] \\ &= \sin(nwt - 2\pi - 2\pi \cdot 2k) \\ &= \sin(nwt) \text{ for all values of } k. \end{aligned}$$

$$\text{Similarly } \sin[n(wt - \frac{4\pi}{3})] = \sin(nwt)$$

The 2<sup>nd</sup> sub-series represents zero sequence system voltage and can be represented by the phasor diagram as shown in figure.

For the 3<sup>rd</sup> sub-series,  $n = 5, 11, 17, \dots = 5 + 6k$ , where  $k = 0 \rightarrow \infty$

$$V_R = \frac{V}{\pi} \left( \frac{v_s}{2} \right) \sum_{n=5,11,17, \dots}^{\infty} \frac{1}{n} \sin(nwt) \quad \xrightarrow{V_R(m)}$$

$$V_Y = \frac{V}{\pi} \left( \frac{v_s}{2} \right) \sum_{n=5,11,17}^{\infty} \frac{1}{n} \sin[n(wt - \frac{2\pi}{3})] \quad \xrightarrow{V_Y(m)}$$

$$V_B = \frac{V}{\pi} \left( \frac{v_s}{2} \right) \sum_{n=5,11,17}^{\infty} \frac{1}{n} \sin[n(wt - \frac{4\pi}{3})] \quad \xrightarrow{V_B(m)}$$

$$\begin{aligned} \text{Now, } \sin[m(wt - \frac{2\pi}{3})] &= \sin[nwt - (5+6k)\frac{2\pi}{3}] \\ &= \sin[nwt - 10\frac{\pi}{3} - 2k \cdot 2\pi] \\ &= \sin[nwt - \frac{4\pi}{3}] \text{ for all values of } k. \\ &= V_B \end{aligned}$$

$$\sin[n(wt - \frac{4\pi}{3})] = \sin[nwt - (5+6k)\frac{4\pi}{3}]$$

The 3<sup>rd</sup> sub-series represents negative sequence system voltage and can be represented by the phasor as shown in figure.

$$\begin{aligned} \text{Now, } V_R &= \frac{V}{\pi} \left( \frac{v_s}{2} \right) \left[ \sum_{n=1,7,13}^{\infty} \frac{1}{n} \sin(nwt) + \sum_{n=3,9,15}^{\infty} \frac{1}{n} \sin(nwt) \right. \\ &\quad \left. + \sum_{n=5,11,17}^{\infty} \frac{1}{n} \sin(nwt) \right] \end{aligned}$$

i.e., Positive sequence + zero sequence + negative sequence.

Line-to-line voltage.

Fourier components of line-to-line voltage can be now calculated as follows:

$$V_{RY} = V_R - V_Y$$

The zero sequence system cancel so that the Fourier components whose frequency is a multiple of three times the inverter frequency (Triplines) are absent.

$$\therefore V_{RY} = \frac{U}{n} \left( \frac{v_s}{2} \right) \sum_{n=1, 7, 13, \dots} \left[ \frac{1}{n} \sin(n\omega t) - \sin(n\omega t - \frac{2\pi}{3}) \right]$$

$$+ \frac{U}{n} \left( \frac{v_s}{2} \right) \sum_{n=5, 11, \dots} \left[ \frac{1}{n} \sin(n\omega t) - \sin(n\omega t - \frac{2\pi}{3}) \right]$$

Here, the frequency spectrum of the line-to-line voltage waveform is similar to that of  $V_R$  but

\* There are no triplines.

\* The amplitude of the remaining components are  $\sqrt{3}$  times greater.

\* The negative sequence components lag by  $60^\circ / (n/3)$  with respect to positive sequence components.

Load neutral voltage:

The voltage of the load neutral ( $V_N$ ) with respect to reference point is a rectangular wave having frequency equal to 3 times that of  $v_R$  and amplitude  $1/3$  that of  $v_R$ . The Fourier components of  $V_N$  are given by

$$V_N = \frac{U}{n} \left( \frac{v_s}{6} \right) \sum_{n=1, 3, \dots} \frac{1}{n} \sin(n\omega t)$$

Load phase voltage:

Fourier components of load voltage (phase) can be calculated as follows

$$V_{RN} = V_R - V_N$$

$$= \frac{U}{n} \left( \frac{v_s}{2} \right) \sum_{n=1, 7, 13, \dots} \frac{1}{n} \sin(n\omega t) - \frac{U}{n} \left( \frac{v_s}{6} \right) \sum_{n=1, 3, \dots} \frac{1}{n} \sin(n\omega t)$$

Thus, the frequency spectrum of the load phase voltage is similar to that of  $V_R$  except that it contains no triplines.

### pulse width modulated inverter:

PIWM inverter is required.

\* to cope with variation with dc input voltage.

\* for voltage regulation.

\* for constant voltage/frequency control.


### Single pulse width modulation:-

In single phase pulse width modulation control,

there is only one pulse per half cycle and the

width of the pulse is varied to control the

inverter output voltage.

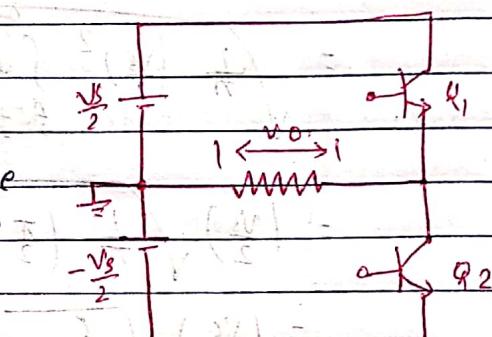

The gate signals for transistors Q<sub>1</sub> & Q<sub>2</sub> are controlled by comparing a rectangular modulating reference signal with a triangular carrier wave.


The control strategy is as follows:

\* If modulating signal (Ar) > carrier signal (Ac) then  $v_o = \frac{v_s}{2}$ .

\* If modulating signal (Ar) < carrier signal (Ac) then  $v_o = -\frac{v_s}{2}$ .

Modulation index is given by
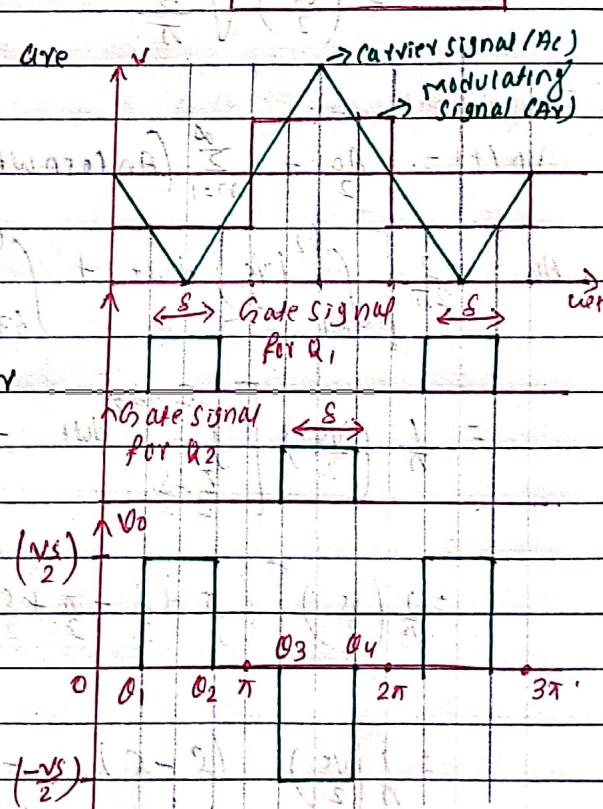
$$M_i = \frac{\text{peak value of modulating signal}}{\text{peak value of carrier signal.}}$$



$$= \frac{Ar}{Ac}$$

$$\text{Now, } \theta_1 = \frac{\pi}{2} - \frac{s}{2} \quad \theta_2 = \frac{\pi}{2} + \frac{s}{2}$$

$$\theta_3 = \frac{3\pi}{2} - \frac{s}{2} \quad \theta_4 = \frac{3\pi}{2} + \frac{s}{2}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{0_1}^{0_2} \left(\frac{Vs}{2}\right)^2 dt + \int_{0_3}^{0_4} \left(-\frac{Vs}{2}\right)^2 dt}$$

$$= \sqrt{\frac{2}{2\pi} \int_{0_1}^{0_2} \left(\frac{Vs}{2}\right)^2 dt}$$

$$= \sqrt{\frac{1}{\pi} \left(\frac{Vs}{2}\right)^2 \int_{\frac{\pi}{2}-\frac{\delta}{2}}^{\frac{\pi}{2}+\frac{\delta}{2}} dt}$$

$$= \left(\frac{Vs}{2}\right) \sqrt{\frac{1}{\pi} \left(\frac{\pi}{2} + \frac{\delta}{2} - \frac{3\pi}{2} + \frac{\delta}{2}\right)}$$

$$= \left(\frac{Vs}{2}\right) \sqrt{\frac{\delta}{\pi}}$$

Fourier Analysis:

$$V_0(t) = A_0 + \sum_{n=1}^{\infty} (A_n \cos n\omega t + B_n \sin n\omega t)$$

$$A_0 = \frac{2}{2\pi} \left[ \int_{0_1}^{0_2} \left(\frac{Vs}{2}\right) d\omega t + \int_{0_3}^{0_4} \left(-\frac{Vs}{2}\right) d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{Vs}{2}\right) \left[ \int_{\frac{\pi}{2}-\frac{\delta}{2}}^{\frac{\pi}{2}+\frac{\delta}{2}} d\omega t - \int_{\frac{3\pi}{2}-\frac{\delta}{2}}^{\frac{3\pi}{2}+\frac{\delta}{2}} d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{Vs}{2}\right) \left[ \left(\frac{\pi}{2} + \frac{\delta}{2} - \frac{\pi}{2} + \frac{\delta}{2}\right) - \left(\frac{3\pi}{2} + \frac{\delta}{2} - \frac{3\pi}{2} + \frac{\delta}{2}\right) \right]$$

$$= \frac{1}{\pi} \left(\frac{Vs}{2}\right) (8 - 8) = 0$$

$$A_n = \frac{2}{2\pi} \left[ \int_{0_1}^{0_2} \left(\frac{Vs}{2}\right) \cos n\omega t \cdot d\omega t + \int_{0_3}^{0_4} \left(-\frac{Vs}{2}\right) \cos n\omega t \cdot d\omega t \right]$$

$$= \frac{1}{\pi} \left(\frac{Vs}{2}\right) \left[ \frac{\sin n\omega t}{n} \Big|_{\frac{\pi}{2}-\frac{\delta}{2}}^{\frac{\pi}{2}+\frac{\delta}{2}} + \frac{\sin n\omega t}{n} \Big|_{\frac{3\pi}{2}-\frac{\delta}{2}}^{\frac{3\pi}{2}+\frac{\delta}{2}} \right]$$

$$= \frac{1}{n\pi} \left( \frac{vs}{2} \right) \left[ -\sin n\left(\frac{\pi}{2} - \frac{\delta}{2}\right) + \sin n\left(\frac{\pi}{2} + \frac{\delta}{2}\right) - \sin n\left(\frac{3\pi}{2} + \frac{\delta}{2}\right) - \sin n\left(\frac{3\pi}{2} - \frac{\delta}{2}\right) \right]$$

$$= \frac{1}{n\pi} \left( \frac{vs}{2} \right) \left[ -\cos n\frac{\delta}{2} + \cos n\frac{\delta}{2} + \cos n\frac{\delta}{2} - \cos n\frac{\delta}{2} \right] \\ = 0$$

$$B_n = \frac{2}{2\pi} \left[ \int_{01}^{02} \left( \frac{vs}{2} \right)^n \sin nwt \cdot dwt + \int_{03}^{04} \left( -\frac{vs}{2} \right)^n \sin nwt \cdot dwt \right]$$

$$= \frac{1}{\pi} \left( \frac{vs}{2} \right) \left[ -\frac{\cos nwt}{n} \Big|_{\frac{\pi-\delta}{2}}^{\frac{\pi+\delta}{2}} + \frac{\cos nwt}{n} \Big|_{\frac{3\pi-\delta}{2}}^{\frac{3\pi+\delta}{2}} \right]$$

$$= \frac{1}{n\pi} \left( \frac{vs}{2} \right) \left[ \cos n\left(\frac{\pi}{2} - \frac{\delta}{2}\right) - \cos n\left(\frac{\pi}{2} + \frac{\delta}{2}\right) + \cos n\left(\frac{3\pi}{2} + \frac{\delta}{2}\right) - \cos n\left(\frac{3\pi}{2} - \frac{\delta}{2}\right) \right]$$

$$= \frac{1}{n\pi} \left( \frac{vs}{2} \right) \left[ \sin n\frac{\delta}{2} + \sin n\frac{\delta}{2} + \sin n\frac{\delta}{2} + \sin n\frac{\delta}{2} \right]$$

$$= \frac{4}{\pi} \left( \frac{vs}{2} \right) \frac{1}{n} \sin n\frac{\delta}{2}$$


$$\text{Then, volt} = \sum_{n=1}^{\infty} \frac{4}{n\pi} \left( \frac{vs}{2} \right) \sin n\frac{\delta}{2} \sin nwt$$

$$\left( \frac{4}{\pi} + \frac{4\pi}{\delta} - \frac{4}{\pi} \cdot \frac{\pi}{\delta} \right) \cdot \frac{4}{\pi} \cdot \left( \frac{vs}{2} \right)$$

Multiple pulse width modulation:

The harmonic content can be reduced by using several pulses in each half cycle of output voltage.
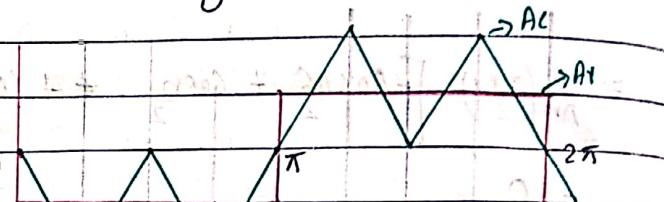
$$\text{Modulation index } (M_i) = \frac{A_v}{A_c}$$



Frequency modulation ratio =

Frequency of carrier signal

Frequency of reference signal ( $\frac{v_s}{2}$ )

$$F_R = \frac{f_c}{f_r}$$

$$\text{Let, 1st, } P = F_R = \text{No. of pulses } \left(\frac{v_s}{2}\right)$$

per half cycle.

Here,

$$\pi = \delta + \pi n = \delta(\frac{1}{2} + n)$$

$$\therefore n = \frac{\pi - \delta}{\delta} = \frac{\pi}{\delta} - 1$$

$$\theta_1 = \frac{(\pi - \delta)}{2}$$

$$\theta_2 = \theta_1 + \delta = \frac{(\pi + \delta)}{2}$$

$$V_{rms} = \sqrt{\frac{2P}{2\pi} \left[ \int_{\theta_1}^{\theta_2} \left(\frac{v_s}{2}\right)^2 d\omega t \right]}$$

$$= \sqrt{\frac{P}{\pi} \left(\frac{v_s}{2}\right)^2 \int_{\theta_1}^{\theta_2} d\omega t}$$

$$= \left(\frac{v_s}{2}\right) \sqrt{\frac{P}{\pi} \cdot \left(-\frac{\pi p}{2} + \frac{\delta}{2} - \frac{\pi p}{2} + \frac{\delta}{2}\right)}$$

$$= \left(\frac{v_s}{2}\right) \sqrt{\frac{P\delta}{\pi}}$$

### Sinusoidal pulse width Modulation..

In this modulation technique, the reference signal is sinusoidal wave.

The control signal is a triangular wave of frequency  $f_c$ . The frequency of sinusoidal reference signal controls the frequency of the output voltage of inverter. The peak value  $A_V$  of the reference signal determines the modulation index.

The carrier and reference waves are mixed in a comparator. When the magnitude of reference signal is more than that of carrier signal, the output of comparator is high and a pulse is generated.

This pulse triggers the thyristor into conduction and a voltage output occurs. It is seen that the width of different output pulses is not the same. The width of the pulses depends on the angular position of the pulse. By varying the modulation index we can vary the rms value of output voltage. If  $\delta_m$  is the width of the  $m^{\text{th}}$  pulse, the rms value of output voltage is

$$V_L = V \left[ \sum_{m=1}^P \frac{\delta_m}{\pi} \right]^{0.5}$$

Where,  $P$  is the number of pulses in one half cycle of output wave.

