

**EXAMPLE 2.5.** A dc supply of 100 V feeds an inductance of 10 H through a thyristor. Find the minimum width of the gate pulse so that the thyristor is triggered. The latching current of thyristor is 80 mA.

**SOLUTION :** The circuit is shown in Fig. 2.9.

$$100 = L \frac{di}{dt}$$

or 
$$i = \frac{100}{10} t = 10 t$$

Thyristor will trigger when  $i = 80 \text{ mA}$ .

$$t = \frac{80 \times 10^{-3}}{10} = 8 \times 10^{-3} \text{ s}$$

Therefore, width of pulse should be more than 8 milli-seconds.

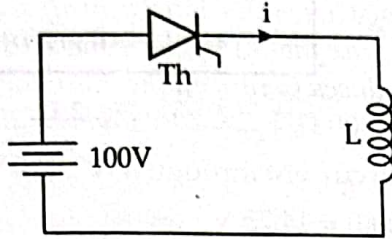


Fig. 2.9.

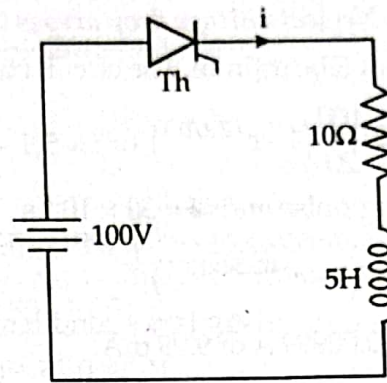


Fig. 2.10.

**EXAMPLE 2.6.** A dc supply of 100 V feeds a load having a resistance of 10 ohms and an inductance of 5 H through a thyristor. The latching current of thyristor is 50 mA. Find the minimum width of the gate pulse.

**SOLUTION :** The circuit is shown in Fig. 2.10. The current at any time  $t$  is

$$i = \frac{100}{10} (1 - e^{-Rt/L}) = 10 (1 - e^{-2t})$$

Thyristor will trigger when  $i = 50 \text{ mA}$

$$50 \times 10^{-3} = 10 (1 - e^{-2t})$$

$$\text{or} \quad e^{-2t} = 0.995$$

$$\text{or} \quad t = 0.0025 \text{ seconds} = 2.5 \text{ milli-seconds}$$

Hence minimum width of gate pulse is 2.5 milli-seconds.

**EXAMPLE 2.7.** Figure 2.11 shows a thyristor circuit. Assume that switch  $S$  is open. The thyristor has a latching current of 40 mA and is fired by a pulse of width 40  $\mu\text{s}$ . (a) Find if the thyristor will turn on (b) The switch is closed. Find the maximum value of  $R$  so that thyristor may turn on.

**SOLUTION :** (a) Switch is open. Resistance  $R$  is not in circuit. The circuit current is

$$i = \frac{90}{25} (1 - e^{-25t/0.5}) = \frac{90}{25} (1 - e^{-50t})$$

At the end of gate pulse, i.e., at  $t = 40 \times 10^{-6} \text{ s}$

$$i = \frac{90}{25} (1 - e^{-50 \times 40 \times 10^{-6}}) = 0.0072 \text{ A}$$

Since the current is less than latching current, the thyristor will not turn on.

$$(b) \quad R = \frac{90}{40 \times 10^{-3} - 0.0072} = 2744 \Omega$$

$R$  should be less than 2744 ohm.

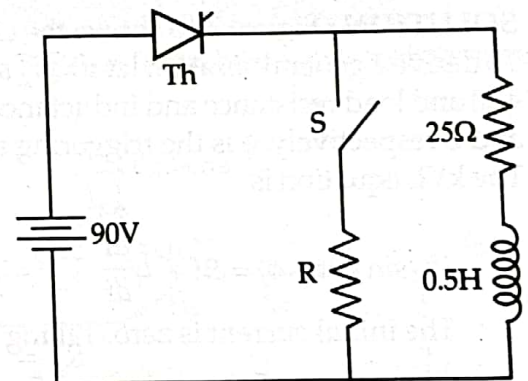


Fig. 2.11.

10.08 W.

**EXAMPLE 2.39.**  $R$ ,  $L$  and  $C$  in an SCR circuit meant for protecting against  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  are  $4\ \Omega$ ,  $6\ \mu\text{H}$  and  $6\ \mu\text{F}$  respectively. If the supply voltage is  $300\ \text{V}$ , find maximum permissible values of  $\frac{dv}{dt}$  and  $\frac{di}{dt}$ .

**SOLUTION:**

$$\left(\frac{di}{dt}\right)_{\max} = \frac{V}{L} = \frac{300}{6 \times 10^{-6}} = 50 \times 10^6\ \text{A/s}$$

When the circuit is switched on the rate of change of voltage across capacitor is given by

$$\frac{dv_C}{dt} = R \frac{di}{dt} + \frac{I_{sc}}{C}$$

$$I_{sc} = \text{short-circuit current} = \frac{300}{4} = 75\ \text{A}$$

Therefore

$$\frac{dv_C}{dt} = 4 \times 50 \times 10^6 + \frac{75}{6 \times 10^{-6}} = 212.5 \times 10^6\ \text{V/s}$$

Hence the maximum permissible value of  $\frac{dv}{dt}$  is  $212.5 \times 10^6\ \text{V/s}$ .



**EXAMPLE 2.37.** In an ac circuit using a thyristor having a  $dv/dt$  rating of  $25 \text{ V}/\mu\text{s}$ , the source inductance is  $0.2 \text{ mH}$ . The rms value of supply voltage is  $230 \text{ V}$ . If the damping factor is  $0.65$ , find the values of  $R$  and  $C$  of the snubber circuit.

**SOLUTION :**

$$V_m = 230 \times \sqrt{2} = 325.27 \text{ V}$$

$$L = 0.2 \times 10^{-3} \text{ H}$$

$$\frac{dv}{dt} = 25 \text{ V}/\mu\text{s} = 25 \times 10^6 \text{ V/s}$$

$$\zeta = 0.65$$

Using Eqn. (2.54)

$$C = \frac{1}{2 \times 0.2 \times 10^{-3}} \left[ \frac{0.564 \times 325.27}{25 \times 10^6} \right]^2 = 134.62 \times 10^{-9} \text{ F}$$

Using Eqn. (2.53)

$$R = 2 \times 0.65 \left[ \frac{0.2 \times 10^{-3}}{134.62 \times 10^{-9}} \right]^{0.5} = 50.1 \Omega .$$