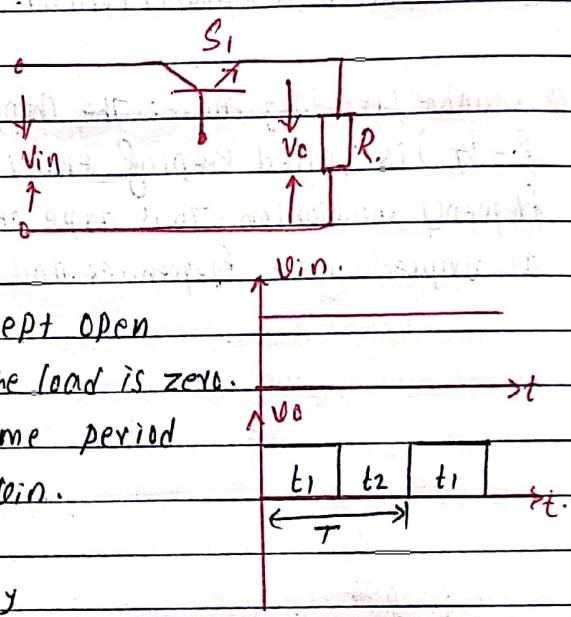


Chopper:

A dc chopper converts dc to dc by changing the effective value. It can be Step-up or Step-down dc voltage. The main principle is to chop a constant dc voltage ( $V_{in}$ ) for a particular time interval and by changing the chopping time, output dc voltage can be controlled. Generally power transistors are used as switch for these purposes.

Step down chopper:

When transistor switch  $S_1$  is closed for a time  $t_1$ , the input voltage  $V_{in}$  appears across the load  $R$ .



If the transistor switch  $S_1$  is kept open for a time  $t_2$ , the voltage across the load is zero.

The average value of  $V_0$  over a time period of  $T$  will be definitely less than  $V_{in}$ .

The average O/P voltage is given by

$$V_0 = \frac{1}{T} \int_0^{t_1} V_{in} \cdot dt$$

$$V_0 = \frac{V_{in} \times t_1}{T}$$

Where,  $t_1$  = transistor on time.

$t_2$  = transistor off time

$$V_0 = \frac{t_1}{t_1 + t_2} \times V_{in} \quad T = \text{time period } (t_1 + t_2)$$

$K = \frac{t_1}{t_1 + t_2}$  duty cycle.

$$\therefore V_0 = K \times V_{in}$$

Assuming loss less transistor switch then,

Input power = Output power

$$P_0 = \frac{1}{T} \int_0^{t_1} V_0 I_0 \cdot dt$$


$$= \frac{1}{T} \int_0^{t_1} \frac{V_0^2}{R} dt = \frac{1}{T} \int_0^{t_1} \frac{V_{in}^2}{R} \cdot dt = \frac{t_1}{T} \frac{V_{in}^2}{R}$$

$$= K \frac{V_{in}^2}{R}$$

The duty cycle can be varied from 0 to 1 by varying  $t_1$  with constant  $T$  or by varying  $T$  with constant  $t_1$  or  $t_2$ .

**Constant frequency mode:** The chopper period  $T$  (or chopping frequency  $f = 1/T$ ) is kept constant and on time  $t_1$  is varied. The width of the pulse is varied and this type of control is known as pulse width modulation (PWM) control.

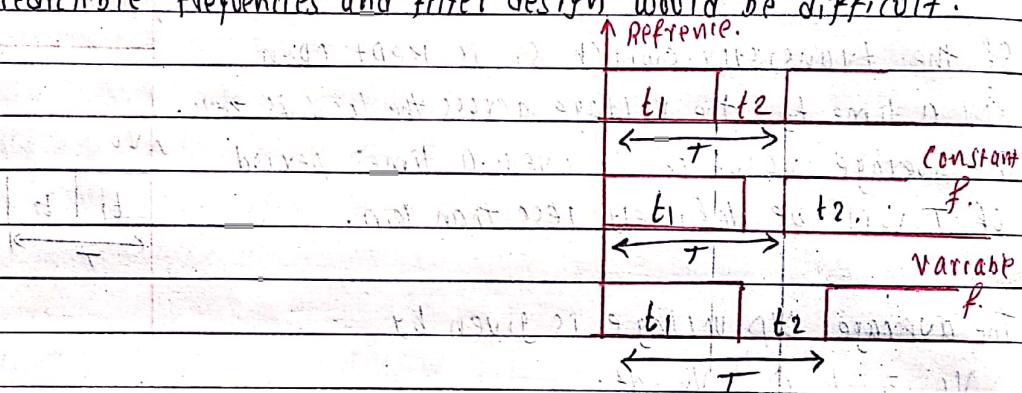**Variable frequency mode:** The chopping period  $T$  (or chopping frequency  $f = 1/T$ ) is varied keeping either  $t_1$  or  $t_2$  constant. This is called frequency modulation. This type of control would generate harmonics at unpredictable frequencies and filter design would be difficult.



Chopper with DC motor as load (RL load)


Let,  $V_{in} = V_m = \text{DC input voltage}$ .

$V_o = \text{DC output voltage (which is applied across the armature of DC motor)}$

$R_a = \text{armature resistance}$ .

$L = \text{Inductance of armature winding.}$

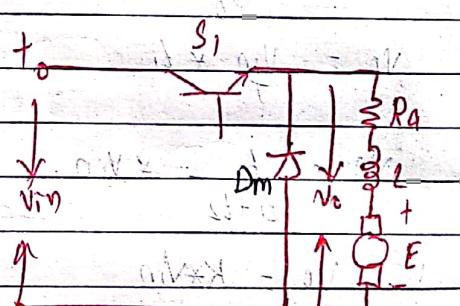$E = \text{Back emf generated by the motor.}$



**Mode-I:** Switching on, current flows through the load.

**Mode-II:** Switch off, the load current continues to flow through free wheeling diode  $D_m$  due to energy stored in the inductor  $L$ .

For mode I:-

$$V_{in} - R_{i01} - L \frac{di_{01}}{dt} - E = 0$$

$$\text{or, } V_{in} - E - R_{i01} = L \frac{di_{01}}{dt}$$

$$\text{or, } \frac{V_{in} - E}{R} - i_{01} = \frac{L}{R} \frac{di_{01}}{dt}$$

$$\text{Let, } y = \frac{V_{in} - E}{R}$$

$$\text{or, } y - i_{01} = \frac{L}{R} \frac{di_{01}}{dt}$$

$$\text{or, } \frac{R}{L} dt = \frac{di_{01}}{(y - i_{01})}$$

Integrating both sides,

$$\int \frac{R}{L} dt = \int \frac{di_{01}}{(y - i_{01})}$$

$$\text{or, } \frac{Rt + K}{L} = -\ln(y - i_{01}) + K_2$$

$$\text{or, } \frac{Rt}{L} = -\ln(y - i_{01}) + K \quad \dots \dots \textcircled{1}$$

$$\text{At, } t=0, i_{01} = I_1$$

$$\text{Then, } K = \ln(I_1) \ln(y - I_1)$$

Now, equation  $\textcircled{1}$  becomes.


$$\frac{Rt}{L} = -\ln(y - i_{01}) + \ln(y - I_1)$$

$$\text{or, } \frac{Rt}{L} = \ln \left( \frac{y - I_1}{y - i_{01}} \right)$$

$$\therefore \frac{y - I_1}{y - i_{01}} = e^{\frac{Rt}{L}}$$

$$\text{or, } y - i_{01} = (y - I_1) e^{-\frac{Rt}{L}}$$
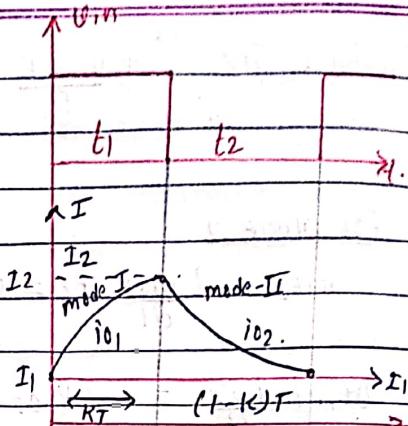
$$\text{or, } i_{01} = y - (y - I_1) e^{-\frac{Rt}{L}} = \frac{V_{in} - E}{R} - \left( \frac{V_{in} - E}{R} - I_1 \right) e^{-\frac{Rt}{L}}$$



$$i_0 = I_1 e^{-R/Lt} + \frac{V_{in}-E}{R} (1 - e^{-\frac{R}{L}t}) \quad - \textcircled{1}$$

For mode 2.

$$Ri_0 + L \frac{di_0}{dt} + E = 0$$

$$\text{or, } L \frac{di_0}{dt} = - (Ri_0 + E)$$

$$\text{or, } \frac{L}{R} \frac{di_0}{dt} = - \left( i_0 + \frac{E}{R} \right)$$

$$\text{or, } \frac{di_0}{- \left( i_0 + \frac{E}{R} \right)} = \frac{R}{L} dt$$

Integrating both sides, we get.

$$\int \frac{di_0}{- \left( i_0 + \frac{E}{R} \right)} = \frac{R}{L} \int dt$$

$$\text{or, } \ln \left( i_0 + \frac{E}{R} \right) + K_1 = - \frac{R}{L} t + K_2$$

$$\text{or, } - \frac{R}{L} t = \ln \left( i_0 + \frac{E}{R} \right) + K \quad \dots \textcircled{2}$$

$$\text{At, } t = 0, i_0 = I_2.$$

$$\therefore K = - \ln \left( I_2 + \frac{E}{R} \right)$$

Then, equation  $\textcircled{2}$  becomes.

$$- \frac{R}{L} t = \ln \left( \frac{i_0 + \frac{E}{R}}{I_2 + \frac{E}{R}} \right)$$

$$\text{or, } \frac{i_0 + \frac{E}{R}}{I_2 + \frac{E}{R}} = e^{-\frac{R}{L}t}$$

$$\text{or, } i_0 = - \left( I_2 + \frac{E}{R} \right) e^{-\frac{R}{L}t} - \frac{E}{R} \quad \dots \textcircled{3}$$

FOR CALCULATING  $I_2$ , PUT  $t = KT$  AT EQUATION (a) AND FOR CALCULATING  $I_1$ , PUT  $t = (1-K)T$  AT EQUATION (b).  
 i.e.,  $i_{01} = I_2$  AT  $t = KT$   
 $i_{02} = I_1$  AT  $t = (1-K)T$

$$\text{Then, } I_{\max} = \frac{V_s}{R} \left[ \frac{1 - e^{-Kz}}{1 - e^{-z}} \right] - \frac{E}{R}$$

$$I_{\min} = \frac{V_s}{R} \left[ \frac{e^{Kz} - 1}{e^z - 1} \right] - \frac{E}{R}$$

### Step Up Chopper:



When the transistor switch is closed an inductor current builds up exponentially.

During this period, inductance  $L$  stores energy and the capacitor  $C$  (which was charged during the previous off period) discharges through load resistance  $R$ . Therefore,  $V_{in}$  load voltage decreases during this period as shown in figure. The

diode  $D_1$  prevents the capacitor discharge back through the switch.

When the transistor switch  $S_1$  is open,

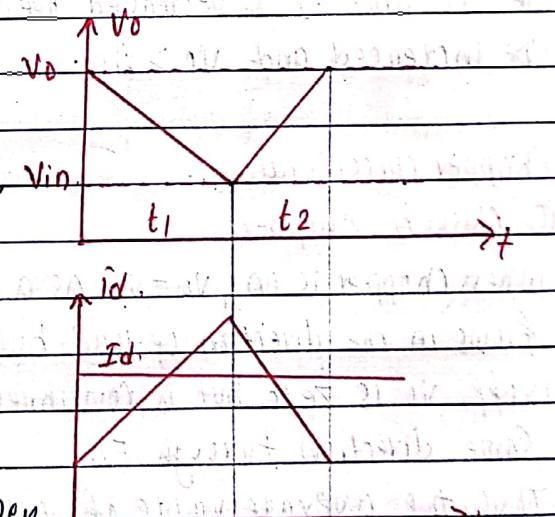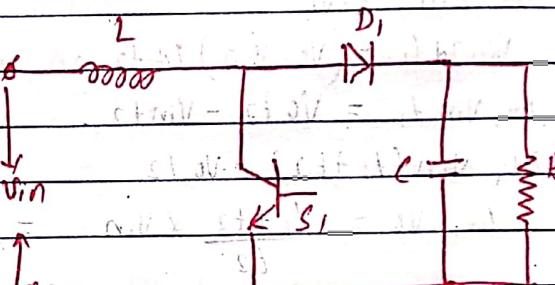the inductor current  $i_d$  flows through  $D_1$ ; thus by charging capacitor  $C$ . The energy released during this period and voltage across capacitor increases. Therefore load voltage  $V_o$  also increases during this period.



Let,  $I_d$  = Average value of inductor current.

$V_o$  = Average value of output voltage.

Then,

Energy input to the inductor during on-time is given by.

$$E_{in} = V_{in} I_d t_1$$

Energy delivered by inductor during off time is given by.

$$E_{out} = (V_o - V_{in}) I_d t_2$$

If the system has no power loss then,

$$E_{in} = E_{out}$$

$$V_{in} I_d t_1 = (V_o - V_{in}) I_d t_2$$

$$\text{Or, } V_{in} t_1 = V_o t_2 - V_{in} t_2$$

$$\text{Or, } V_{in}(t_1 + t_2) = V_o t_2$$

$$\text{Or, } V_o = \frac{t_1 + t_2}{t_2} \times V_{in} = \frac{T}{t_2} V_{in}$$

If off time  $t_2$  is decreased keeping  $(t_1 + t_2)$  constant, then  $V_o$  will be increased and  $V_o > V_{in}$ .

Chopper classification:

① Class A chopper:

When chopper is on,  $V_o = V_{in}$  as a result the current flows in the direction of load but when the chopper is off,  $V_o$  is zero but it continues to flow in the same direction through FD.


Thus, the average value of output voltage and current will always be positive and output will be seen only in first quadrant. In Class A chopper, power will always flow from source to load as average voltage  $V_o$  is less than input voltage  $V_{in}$ .

### ② Class-B-chopper.

When the chopper is ON,  $V_o$  is zero but the load voltage  $E$  drives the current through the inductor  $L$ . Inductor stores energy.

during ON time of the chopper i.e.  $E > V_o$  and during OFF time current stored in inductor flows through diode  $D_2$  to the source.

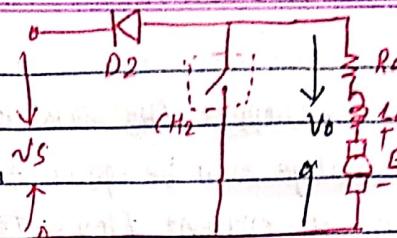No matter the chopper is ON or OFF, current will always flow through the load so the current always treated as negative.




Since,  $V_o$  is +ve and  $I_o$  is -ve, power will flows from load to source. Since load voltage is more than source voltage such choppers are called Step up chopper.
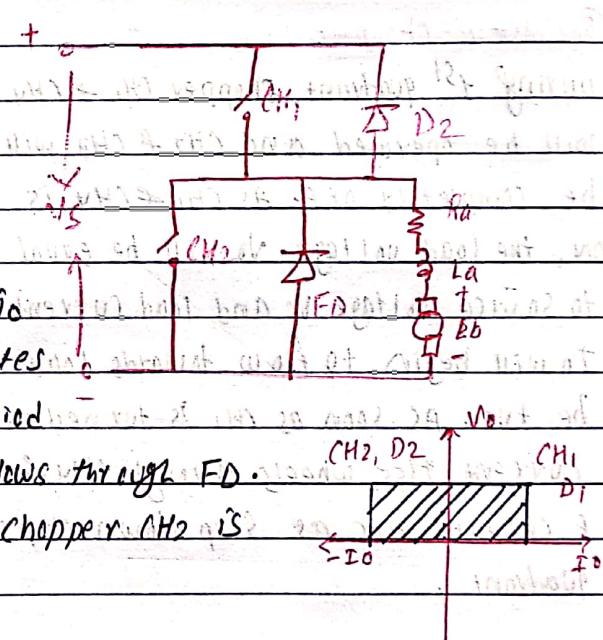
### ③ Class-C chopper.

In 1<sup>st</sup> quadrant operation,  $CH_1$  is turned ON keeping  $CH_2$  OFF, the current will flow in the path  $V_S - CH_1 - \text{Load} - V_S$ . Here  $V_o$  and  $I_o$  are +ve therefore motor operates in 1<sup>st</sup> quadrant. During ON period of  $CH_1$ , the armature current will flow through  $F_D$ .


In this 1<sup>st</sup> quadrant operation, chopper  $CH_2$  is completely turned OFF.




In 2<sup>nd</sup> quadrant,  $CH_2$  is turned ON keeping  $CH_1$  turned OFF. During ON time of  $CH_2$ ,  $E$  drives the current through inductor and when  $CH_2$  is OFF, current flows towards source and current is negative and hence dc motor operates in 2<sup>nd</sup> quadrant.
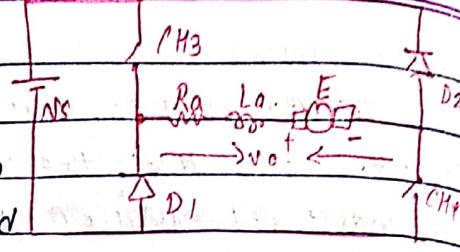
### ① Class D chopper:

When both chopper  $CH_3$  &  $CH_4$  are ON, the output voltage will be equals to  $V_s$  and when  $CH_3$  is OFF current flows through  $D_1$  and hence average value of output current and voltage is always positive. I.e. 1st quadrant operation.




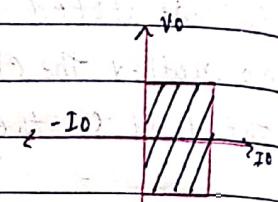When both the Chopper  $CH_3$  &  $CH_4$  are OFF, the diode  $D_1$  and  $D_2$  starts conducting. Here  $E$  is greater than  $V_s$ . but the load current is +ve that charges the source. The current will flow in the path  $D_2 - V_s - n - E - D_2$  and hence output voltage becomes  $-V_o$ . So, the dc motor operates in a 4th quadrant.


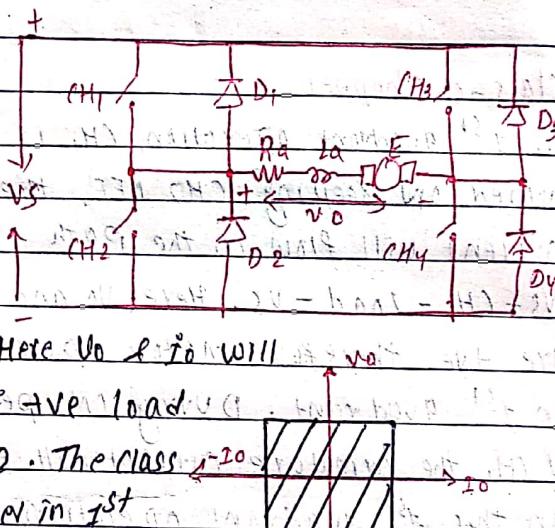
### ② Class E chopper:

During 1st quadrant, chopper  $CH_1$  &  $CH_4$  will be operated and  $CH_2$  &  $CH_3$  will be completely OFF. As  $CH_1$  &  $CH_4$  is ON, the load voltage  $V_o$  will be equal to Source voltage  $V_s$  and load current  $i_o$  will begin to flow towards load. Here  $V_o$  &  $i_o$  will be +ve. As soon as  $CH_1$  is turned OFF even load current free wheels through  $CH_4$  &  $D_2$ . The class E chopper acts as Step Down chopper in 1st quadrant.



During 2nd quadrant,  $CH_2$  is operated and other 3-choppers are kept off. As  $CH_2$  is ON, -ve current starts to flow from  $E$ . Energy stored in inductor  $L$ , when  $CH_2$  is ON. When  $CH_2$  is OFF, current move back to the source through  $D_1$  to produce Second quadrant operation of dc motor. The class E acts as Step-up chopper in 2nd quadrant.

In 3<sup>rd</sup> quadrant operation CH<sub>2</sub> & CH<sub>3</sub> is operated and CH<sub>4</sub> & CH<sub>1</sub> are kept OFF. For this quadrant working polarity of load should be reversed. As chopper CH<sub>3</sub> is ON load gets connected to source in the path VS - CH<sub>3</sub> - E - CH<sub>2</sub> - VS and hence V<sub>L</sub> and I<sub>L</sub> will be -ve. In this case chopper acts as step down chopper.

CH<sub>4</sub> will be completely OFF. When CH<sub>4</sub> is ON, current will starts to flow CH<sub>4</sub> - D<sub>2</sub> - E and inductor will store the energy. As CH<sub>4</sub> is turned OFF current is feedback to the source through D<sub>2</sub> and D<sub>3</sub> and the operation will be in 4<sup>th</sup> quadrant.