

## Rectifiers:

The conversion of ac to dc is known as rectification. Diode rectifiers are known as uncontrolled rectifiers because for a fixed value of ac input voltage, the output dc voltage is fixed and cannot be changed.

Rectifiers circuit using thyristors are known as controlled rectifiers. By changing the firing angle of thyristor the output dc voltage can be controlled.

### Single phase half wave uncontrolled rectifiers.

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(wt) d(wt)$$

$$= \frac{V_m}{2\pi} \left[ \int_0^{\pi} V_m \sin(wt) dt + \int_{\pi}^{2\pi} 0 d(wt) \right]$$

$$= \frac{V_m}{2\pi} (-\cos(wt)) \Big|_0^{\pi}$$

$$= \frac{V_m}{2\pi} (1+1)$$






$$= \frac{V_m}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin(wt))^2 d(wt) + \int_{\pi}^{2\pi} 0 d(wt)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \left( \frac{1-\cos(2wt)}{2} \right) d(wt)}$$
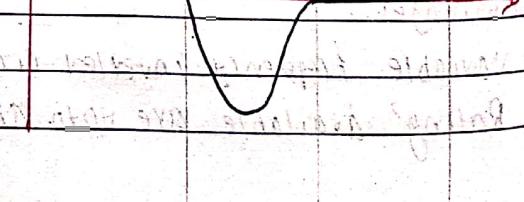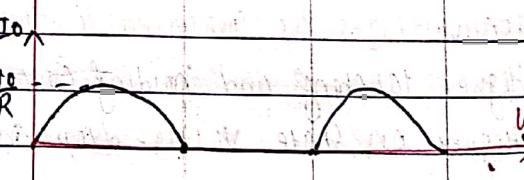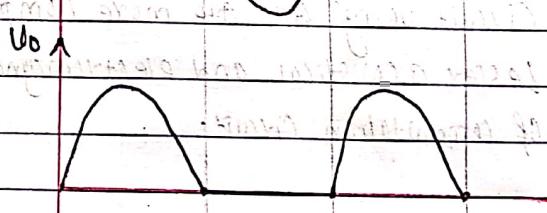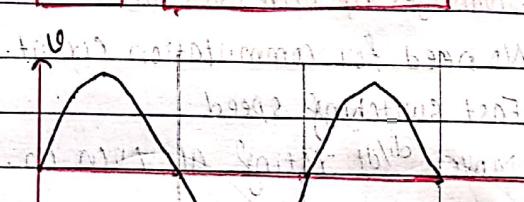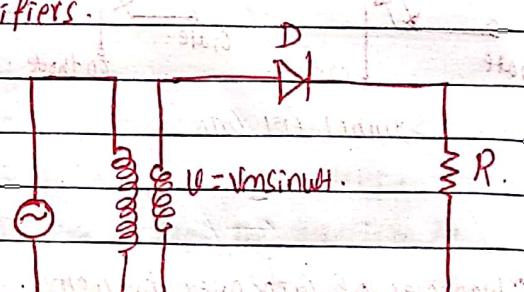
$$= \sqrt{\frac{V_m^2}{4\pi} \left[ wt - \frac{\sin(2wt)}{2} \right]_0^{\pi}}$$



$$= \left[ \frac{V_m^2}{4\pi} \left( \pi - \frac{\pi \sin \pi}{2} - 0 + \frac{\pi \sin 0}{2} \right) \right]^{1/2}$$

$$= \left[ \frac{V_m^2 \cdot \pi}{4\pi} \right]^{1/2} = \frac{V_m}{2}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{2R}$$

$$DC \text{ Power } (P_{dc}) = V_{dc} I_{dc} = \frac{V_m^2}{\pi^2 R}$$

$$AC \text{ Power } (P_{ac}) = V_{rms} I_{rms} = \frac{V_m^2}{4R}$$

$$\text{Rectification efficiency } (\eta) = \frac{P_{dc}}{P_{ac}} = \frac{V_m^2}{\pi^2 R} \times \frac{VR}{V_m^2} = \frac{4}{\pi^2} = 40.5\%$$

Effective ( $V_{rms}$ ) value of ac component of output voltage is

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} = \sqrt{\frac{V_m^2}{4} - \frac{V_m^2}{\pi^2}} = V_m \sqrt{1 - \frac{1}{\pi^2}} = 0.3855 V_m$$

$$\text{Form factor (FF)} = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{2} \times \pi}{V_m} = \frac{\pi}{2} = 1.57$$

$$\text{Ripple factor (RF)} = \frac{V_{ac}}{V_{dc}} = \frac{0.3855 V_m \times \pi}{V_m} = 1.21$$

$$= \sqrt{F.F^2 - 1} = \sqrt{1.57^2 - 1} = 1.21$$

If  $V_s$  and  $I_s$  are the rms voltage and current at the secondary of the transformer feeding the rectifier circuit, transformer utilization factor (CTUF) is given by,

$$CTUF = \frac{P_{dc}}{V_s I_s} = \frac{\frac{V_m}{\pi} \times \frac{V_m}{\pi R}}{\frac{V_m}{\sqrt{2}} \times \frac{V_m}{\sqrt{2} R}} \Rightarrow \frac{2\sqrt{2}}{\pi^2} = 0.2865 = 28.65\%$$

$$\text{Input power factor (P.F)} = \frac{I_s \cos \theta}{I_s} = \cos \theta$$

Single phase half wave uncontrolled rectifier with R-L loads.

$$V_{DC} = \frac{1}{2\pi} \left[ \int_0^{\pi+\alpha} V_m \sin \omega t \, d\omega t + \int_{\pi+\alpha}^{2\pi} 0 \, d\omega t \right]$$

$$= \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_0^{\pi+\alpha} \right]$$

$$= \frac{V_m}{2\pi} \left[ -(\cos(\pi+\alpha) + \cos 0) \right]$$

$$= \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_{DC} = V_{DC} = \frac{V_m}{R} (1 + \cos \alpha)$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi+\alpha} (V_m \sin \omega t)^2 \, d\omega t + \int_{\pi+\alpha}^{2\pi} 0 \, d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi+\alpha} (1 - \cos 2\omega t) \cdot d\omega t}$$










$$= \sqrt{\frac{V_m^2}{4\pi} \left[ \omega t - \frac{1}{2} \sin \omega t \Big|_0^{\pi+\alpha} \right]}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left( (\pi+\alpha) - \frac{\sin(\pi+\alpha)}{2} \right)}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left( (\pi+\alpha) + \frac{\sin \alpha}{2} \right)}$$


$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left[ \left( \frac{\pi+\alpha}{2} \right) + \frac{\sin \alpha}{2} \right]}$$

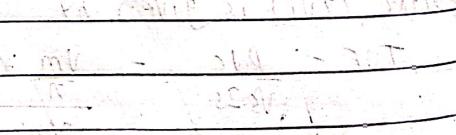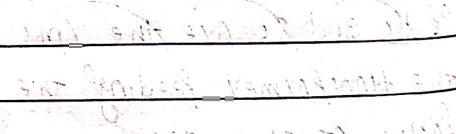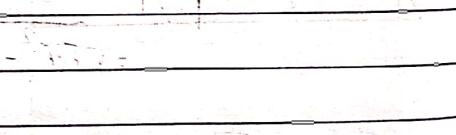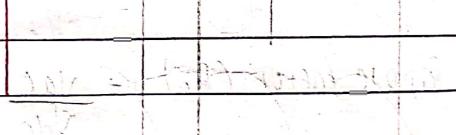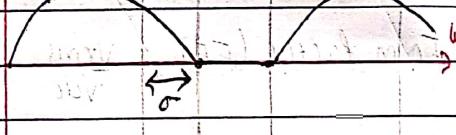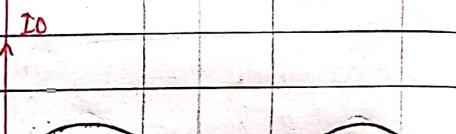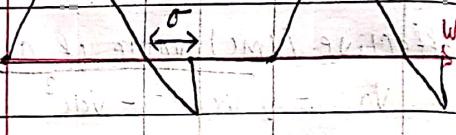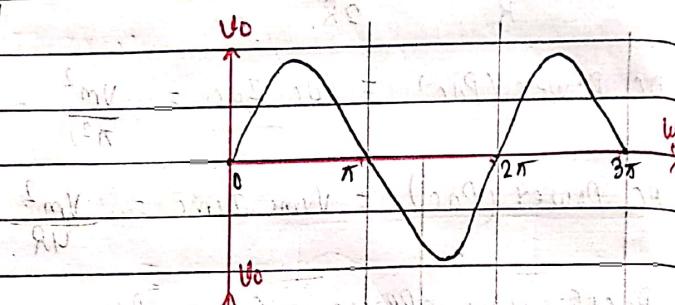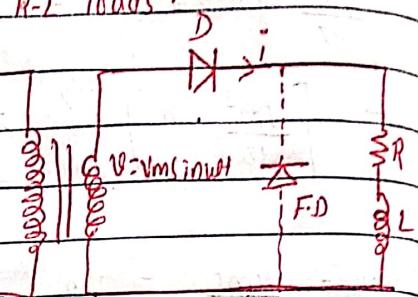The value of  $\alpha$  depend on the ratio  $R_L$ .



The average Voltage and current can be increased by making  $\sigma = 0.98$ . A free wheeling diode (FD) is connected across the load. This can be achieved. The free wheeling diode FD does not allow the negative voltage to appear across the load. At  $wt = \pi$  the current from diode is transferred to FD.

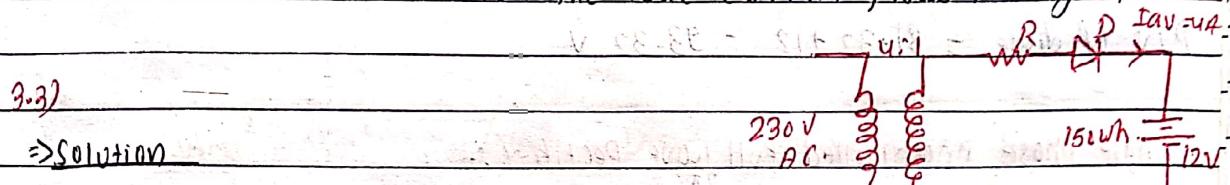From  $wt = \pi$  to  $wt = \pi + \sigma$  the load current flows through F.D.



Q.3)

SOLUTION

The peak value of input secondary voltage

$$= \frac{230 \times \sqrt{2}}{\sigma} = 81.32 \text{ V}$$

Now, the diode starts to conduct when

$$81.32 \sin wt = 12$$

$$wt = \sin^{-1}\left(\frac{12}{81.32}\right) = 8.49^\circ$$

Here, the diode conducts  $8.49^\circ$  to  $(180 - 8.49^\circ)$

$$= 8.49^\circ \text{ to } 171.51^\circ$$

$$V_{dc} = \frac{1}{2\pi} \int_{8.49}^{171.51} (81.32 \sin wt - 12) d(wt)$$

$$= 20.167 \text{ V}$$

$$I_{dc} = \frac{V_{dc}}{R} \Rightarrow R = \frac{V_{dc}}{I_{dc}} = \frac{20.167}{4} = 5.04 \Omega$$

$$V_{rms} = \left[ \frac{1}{2\pi} \int_{8.49}^{171.51} (81.32 \sin wt - 12)^2 d(wt) \right]^{1/2} = 33.192 \text{ V}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{33.192}{5.04} = 6.585 \text{ A}$$

$$P_{dc} = 12 \times 4 = 48$$

$$\text{Power rating of } R = I_{rms}^2 R = (6.585)^2 \times 5.04 = 218.6 \text{ W}$$

Here,  $U_8 \times$  charging time = 150

$$\therefore \text{Charging time} = \frac{150}{48} = 3.125 \text{ hours}$$

$$\text{Rectifier efficiency} = \frac{P_{dc}}{P_{dc} + I_{rms}^2 R} = \frac{U_8 \times 100\%}{U_8 + 2I \cdot R \cdot B} = 18\%$$

$$PIV \text{ of diode} = 81.32 + 12 = 93.32 \text{ V}$$


Single phase uncontrolled Full wave Rectifier :-

$$V_{dc} = \frac{1}{2\pi} \int_0^\pi V_m \sin(wt) d(wt) + \int_\pi^{2\pi} V_m \sin(wt) d(wt)$$

$$= \frac{1}{\pi} \int_0^\pi V_m \sin(wt) d(wt)$$

$$= \frac{V_m}{\pi} - \cos(wt) \Big|_0^\pi$$

$$= \frac{2V_m}{\pi}$$

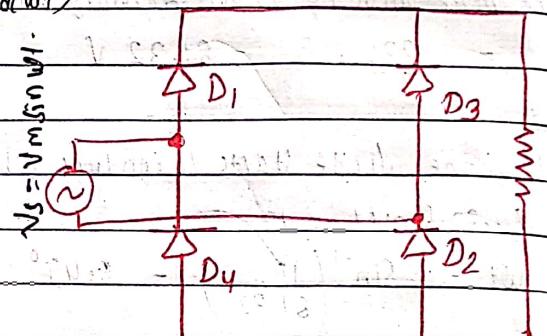

$$I_{dc} = \frac{V_{dc}}{R} = \frac{2V_m}{\pi R}$$

$$P_{dc} = V_{dc} I_{dc} = \frac{4V_m^2}{\pi^2 R}$$




$$V_{rms} = \left[ \frac{1}{\pi} \int_0^\pi (V_m \sin(wt))^2 d(wt) \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{\pi} \int_0^\pi (1 - \cos 2wt)^2 d(wt) \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \left( \int_0^\pi (1 - \cos 2wt)^2 d(wt) \right) \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} (2\pi - 0 + 0 - 0) \right]^{1/2}$$

$$= \frac{V_m}{\sqrt{2}}$$

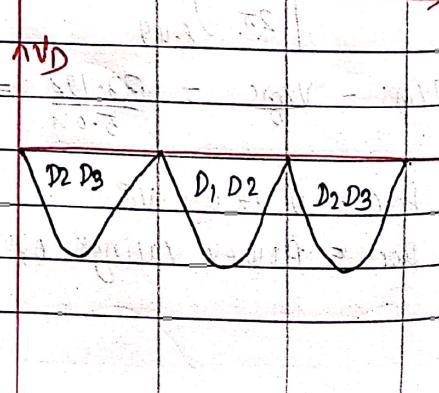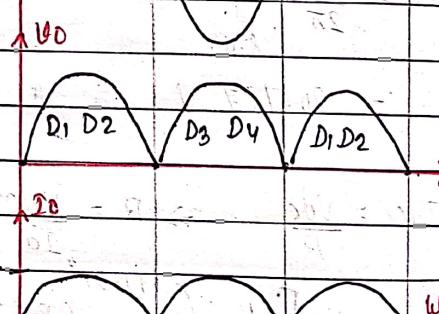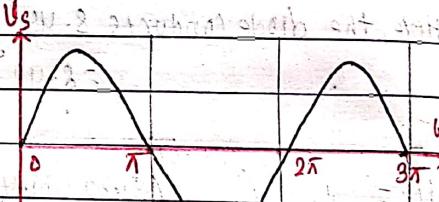

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{Vm}{\sqrt{2}R}$$

$$P_{\text{dc}} = V_{\text{rms}} I_{\text{rms}} = \frac{Vm}{\sqrt{2}} \times \frac{Vm}{\sqrt{2}R} = \frac{Vm^2}{2R}$$

$$\text{Rectification efficiency } (\eta) = \frac{P_{\text{dc}}}{P_{\text{ac}}} = \frac{\frac{1}{2}Vm^2 \times 2R}{Vm^2} = \frac{8}{\pi^2} = 81.05\%$$

$$V_{\text{dc}} = \sqrt{V_{\text{rms}}^2 - V_{\text{ac}}^2} = \sqrt{\frac{Vm^2}{2} - \frac{4Vm^2}{\pi^2}} = Vm \sqrt{\frac{1}{2} - \frac{4}{\pi^2}} \\ = 0.3078 Vm$$

$$\text{Form factor} = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{Vm}{\sqrt{2}} \times \frac{2Vm}{\pi} = \frac{Vm}{\sqrt{2}} \times \frac{\pi}{2Vm} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$\text{Ripple factor} = \frac{V_{\text{ac}}}{V_{\text{dc}}} = \frac{0.3078 Vm}{\frac{2Vm}{\pi}} \Rightarrow 0.3078 \times \frac{\pi}{2} = 0.4849$$

$$\text{PIV} = Vm$$

Advantages of bridge rectifier circuit over centre tapped transformer rectifier

- It does not require a centre tapped transformer.
- The peak inverse voltage in bridge circuit is half of that in the full wave circuit using centre tapped transformer.

#### Disadvantages of bridge rectifier circuit

- It requires 4 diodes as compared to 2 in the other circuit.
- In a bridge circuit two diodes are always in circuit (in both positive and negative half cycles). In the circuit using centre tapped transformer only one diode is in circuit at one time. Therefore, bridge circuit has more voltage drop, more losses, poor efficiency and power voltage regulation as compared to the circuit using centre tapped transformer. Therefore bridge circuit is more suitable for high voltages.

Single phase half wave controlled rectifier.

$$V_{dc} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t + \int_{\pi}^{2\pi} 0 \, d\omega t \right]$$

$$= \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t - \cos \omega t \, d\omega t$$

$$= \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\pi} \right] = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$\therefore V_{dc} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R}$$

$$V_{rms} = \left[ \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 \, d\omega t + \int_{\pi}^{2\pi} 0 \, d\omega t \right] \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \frac{(1 - \cos 2\omega t)}{2} \, d\omega t \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{4\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \Big|_{\alpha}^{\pi} \right] \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{4\pi} \left[ \frac{(\pi - \alpha)}{2} - \frac{\sin 2\alpha}{2} + \frac{\sin 2\pi}{2} \right] \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{4\pi} \left[ \frac{(\pi - \alpha)}{2} + \frac{\sin 2\alpha}{2} \right] \right]^{1/2}$$

$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left[ \frac{(\pi - \alpha)}{2} + \frac{\sin 2\alpha}{2} \right]}$$

$$I_{rms} = \frac{V_{rms}}{R}$$

If firing angle ( $\alpha$ ) =  $0^\circ$ , then.

$$V_{DC} = \frac{V_m}{2\pi} (1+1) = \frac{V_m}{\pi}$$

$$V_{RMS} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left( (\pi - 0) + \sin 2x_0 \right)} = \frac{V_m}{2}$$

If firing angle  $\alpha = 180^\circ$  both  $V_{DC}$  &  $V_{RMS}$  are zero.

The input current is the same as rms load current.

3.9) =>

The thyristor will conduct when the instantaneous value of ac voltage is more than 50 V.

$$100 \sin \omega t = 50$$

$$\omega t = \sin^{-1} \left( \frac{50}{100} \right) = 30^\circ = \frac{\pi}{6}$$

Conduction angle is from  $30^\circ$  to  $(180 - 30^\circ) = 150^\circ$  i.e.  $\frac{\pi}{6}$  to  $\frac{5\pi}{6}$

$$\text{Now, current through the circuit} = \frac{1}{2\pi} \int_{\pi/6}^{5\pi/6} (100 \sin \omega t - 50) d\omega t$$

$$= 1.089 \text{ A.}$$

Single phase half wave controlled rectifier with R-L load.

$$V_{dc} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) \right]$$

$$= \frac{V_m}{2\pi} (1 - \cos \alpha)$$

$$= \frac{V_m}{2\pi} (1 + \cos \alpha)$$





$$\text{Average load current } I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

During the time period I:  $\alpha < \omega t < \pi$ , SCR conducts.


During the period II:  $\pi < \omega t < 2\pi + \alpha$ , FD conducts.

During the interval  $\alpha < \omega t < \pi$ , the source supplies power to the load.

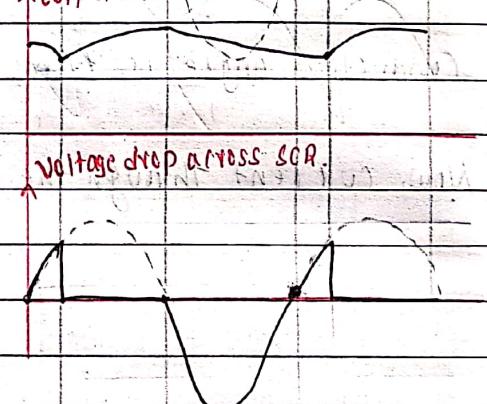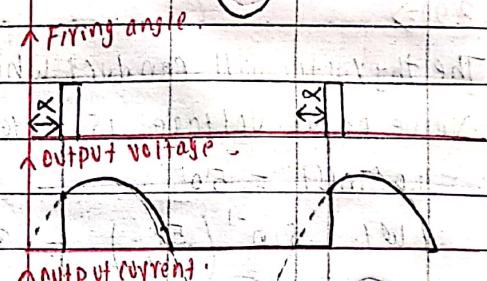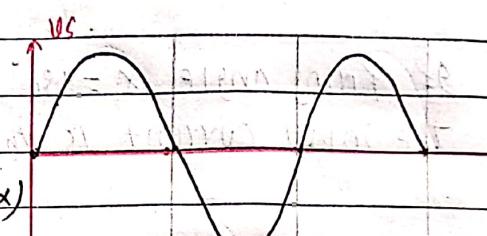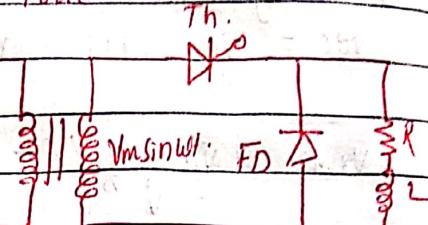During the interval  $\pi < \omega t < 2\pi + \alpha$ , the energy stored in inductance is supplied to load resistance.



If F-D is not used, then

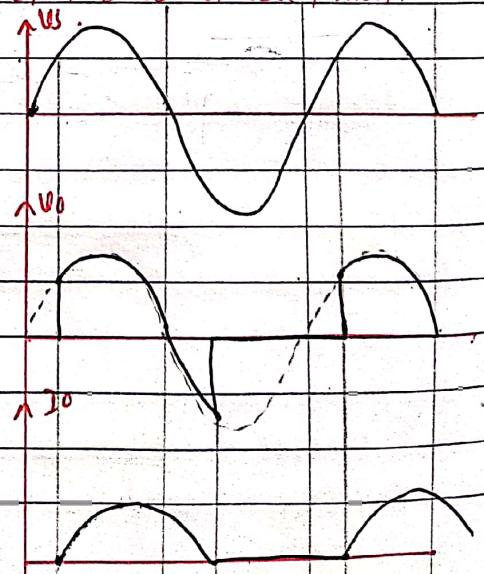

### Single phase full wave controlled rectifier

It is also known as full converter.

During the positive half cycle thyristor  $Th_1$ ,

&  $Th_2$  are forward biased. When  $Th_1$  &  $Th_2$  are fired at  $\omega t = \alpha$ , they start conducting and

Supplying the load current. At  $\omega t = \pi$ , current

is zero, the supply voltage reverses and

$Th_1$  &  $Th_2$  are turned off by natural commutation.

In negative half cycle  $Th_3$  &  $Th_4$  conduct

from  $\omega t = \pi + \alpha$  to  $\omega t = 2\pi$ . At  $\omega t = 2\pi$ ,

current is zero, the supply voltage

reverses and  $Th_3$  &  $Th_4$  are turned off

by natural commutation.

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$


$$= \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left( \omega t - \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\pi}}^{1/2}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left( \pi - \alpha - 0 + \frac{\sin 2\alpha}{2} \right)}^{1/2}$$
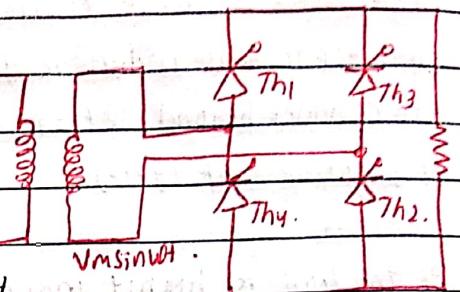
$$= V_m \sqrt{\frac{1}{2\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$



↑ Fixing angle of  $Th_1$  &  $Th_2$ .

↑ Fixing angle of  $Th_3$  &  $Th_4$ .

↓ Output voltage

↓ Output current

↓ Voltage drop across  $(Th_1 \& Th_2)$

↓ Voltage drop across  $(Th_3 \& Th_4)$

↓ Output current

↓

↓

↓

↓

Single phase Full wave controlled Rectifier with R-L load.

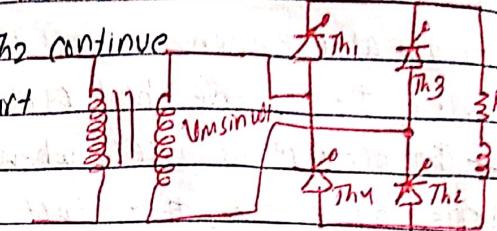Since the load is inductive thyristor  $Th_1$  &  $Th_2$  continue to conduct beyond  $wt = \pi$  i.e. during part of negative half cycle.



If the load is highly inductive, the time constant  $L/R$  is very high and remains more or less constant.


$$\text{Average output voltage } (V_{dc}) = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin wt \cdot dwt$$

$$= \frac{V_m}{\pi} \left[ -\cos wt \right]_{\alpha}^{\pi+\alpha}$$

$$= \frac{V_m}{\pi} \left[ -\cos(\pi+\alpha) + \cos\alpha \right]$$

$$= \frac{2V_m}{\pi} \cos\alpha$$

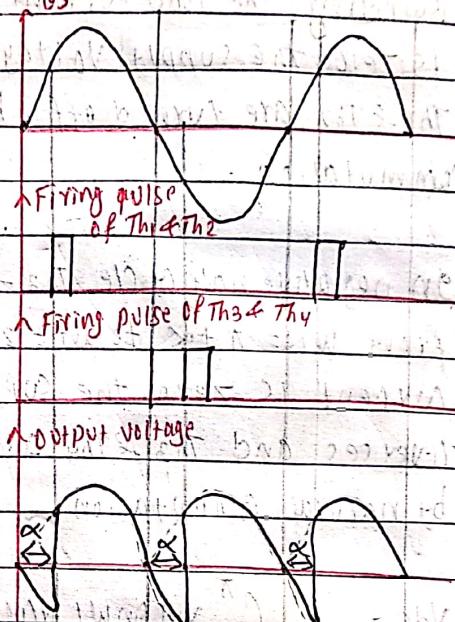$V_{dc}$  can be varied from  $2V_m/\pi$  to  $-2V_m/\pi$  by varying  $\alpha$  from  $0$  to  $\pi$ .



$$V_{dc} = \left[ \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 wt \, dwt \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \left[ wt - \frac{\sin 2wt}{2} \right] \Big|_{\alpha}^{\pi+\alpha} \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \left[ (\pi+\alpha - \alpha) - \frac{\sin 2(\pi+\alpha)}{2} + \frac{\sin 2\alpha}{2} \right] \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \left( \pi - \frac{\sin 2\alpha + \sin 2\pi}{2} \right) \right]^{1/2}$$

$$= \frac{V_m}{\sqrt{2}}$$

### Three phase half wave diode rectifier.

It is fed by a delta-star transformer

from 3-phase mains supply. 3-phase  
It can be considered as three SUPPLY.


Single phase half wave rectifiers

combined together. The diode in any

phase conducts when the voltage of that phase is

higher than that on the other two phases. In this

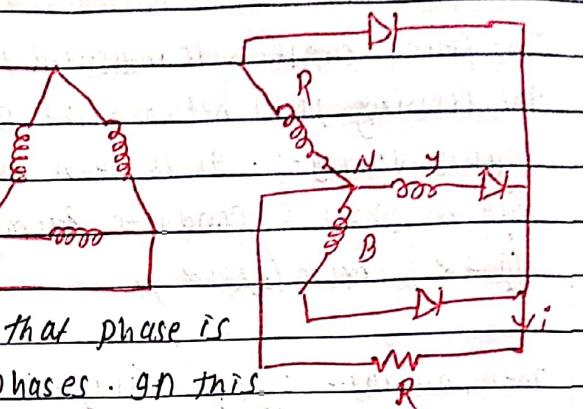rectifier, each diode conducts for  $120^\circ$ .



The diode in Phase R conducts from  $\pi$  to

$5\pi/6$ . If line to neutral voltage of

phase R is given by  $V_{m \sin \theta}$ , then

Average Output Voltage  $V_{dc}$  is.

$$V_{dc} = \frac{1}{(2\pi)} \int_{\pi/6}^{5\pi/6} V_{m \sin \theta} d\theta$$

$$= \frac{3Vm}{2\pi} \left[ -\cos \theta \right]_{\pi/6}^{5\pi/6}$$

$$= \frac{3Vm}{2\pi} (\sqrt{3})$$

$$= \frac{3\sqrt{3}Vm}{2\pi}$$


$$Vm_{ms} = \left[ \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_{m^2 \sin^2 \theta} d\theta \right]^{1/2}$$

$$= \left[ \frac{3Vm^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_{\pi/6}^{5\pi/6} \right]^{1/2}$$

$$= \left[ \frac{3Vm^2}{4\pi} \left( \frac{5\pi}{6} - \frac{\pi}{6} \right) + \left( \frac{\sin 2\pi/6}{2} - \frac{\sin 2\pi \times 5\pi/6}{2} \right) \right]^{1/2}$$


$$= \left[ \frac{3Vm^2}{4\pi} \left( \frac{2\pi}{3} + \frac{\sqrt{3}}{4} + \frac{\sqrt{3}}{4} \right) \right]^{1/2}$$
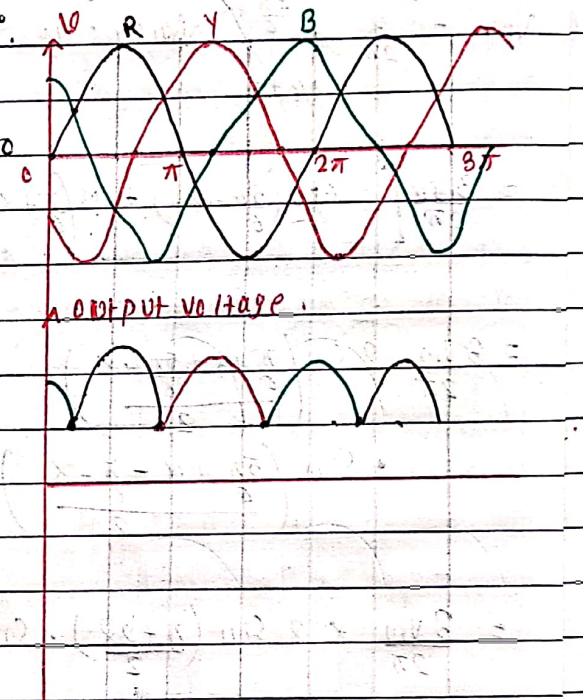
$$= \frac{3Vm^2}{4\pi} \left( \frac{2\pi}{3} + \frac{\sqrt{3}}{2} \right)^{1/2} = 0.84Vm$$


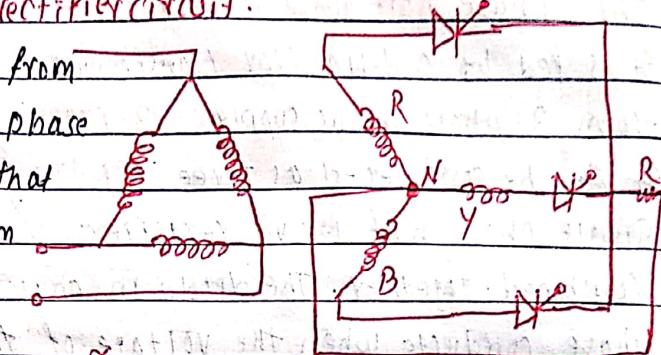
### Three phase half wave controlled rectifier circuit.

The firing angle  $\alpha$  is measured from the crossing point between the phase supply voltages. It is seen that SCR in phase R conducts from  $(\frac{\pi}{6} + \alpha)$  to  $(5\pi/6 + \alpha)$ .



Then, average output voltage

$$V_{oh} = \frac{3}{2\pi} \int_{\pi/6 + \alpha}^{5\pi/6 + \alpha} V_m \sin \omega d\omega$$

$$= \frac{3V_m}{2\pi} \left[ -\cos\left(\frac{5\pi}{6} + \alpha\right) + \cos\left(\frac{\pi}{6} + \alpha\right) \right]$$

$$= \frac{3V_m}{2\pi} \cdot 2 \sin\left(\frac{\pi - \alpha + 5\pi - \alpha}{6}\right)$$


$$\cdot \sin\left(\frac{5\pi + \alpha - \pi - \alpha}{6}\right)$$

$$= \frac{3V_m}{2\pi} \cdot 2 \sin\left(\frac{\pi + 2\alpha}{2}\right) \cdot \sin\left(\frac{2\pi}{3}\right)$$

$$= \frac{3V_m}{2\pi} \cdot 2 \sin\left(\frac{\pi + \alpha}{2}\right) \cdot \sin\left(\frac{\pi}{3}\right)$$

$$= \frac{3V_m}{\pi} \cos\alpha \cdot \frac{\sqrt{3}}{2}$$
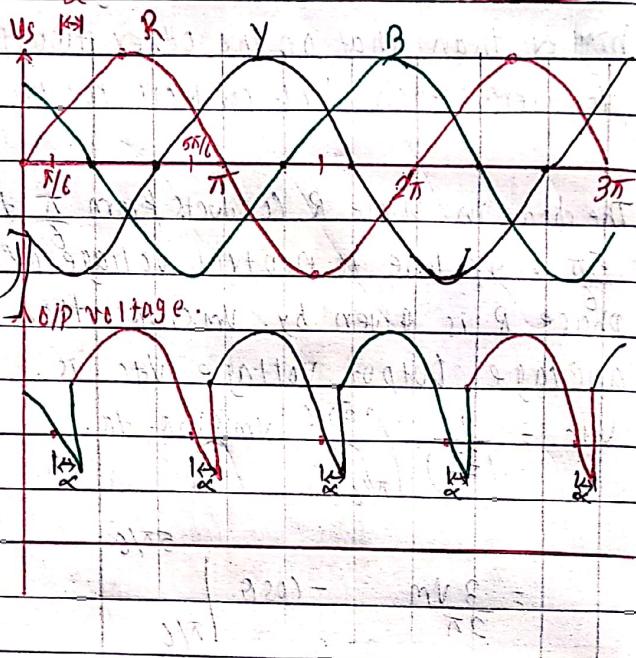
$$= \frac{3\sqrt{3}V_m \cos\alpha}{2\pi}$$



### Three phase full wave rectifier circuit.

$T_{h1}, T_{h2} \& T_{h3}$  form the positive group.

$D_1, D_2 \& D_3$  form the negative group.

The thyristor are fired at intervals of  $120^\circ$ . At one time thyristor and one diode conduct.

Let line to neutral voltages be

written as,

$$V_{an} = V_m \sin(\omega t)$$

$$V_{bn} = V_m \sin(\omega t - 120^\circ)$$

$$V_{cn} = V_m \sin(\omega t - 240^\circ)$$

The line to line voltages are.

$$V_{ac} = V_{an} - V_{cn}$$



$$= V_m \sin \omega t - V_m \sin(\omega t - 240^\circ)$$

$$= \sqrt{3} V_m \sin(\omega t - 30^\circ)$$

$$V_{ba} = \sqrt{3} V_m \sin(\omega t + 150^\circ)$$

$$V_{cb} = \sqrt{3} V_m \sin(\omega t + 90^\circ)$$
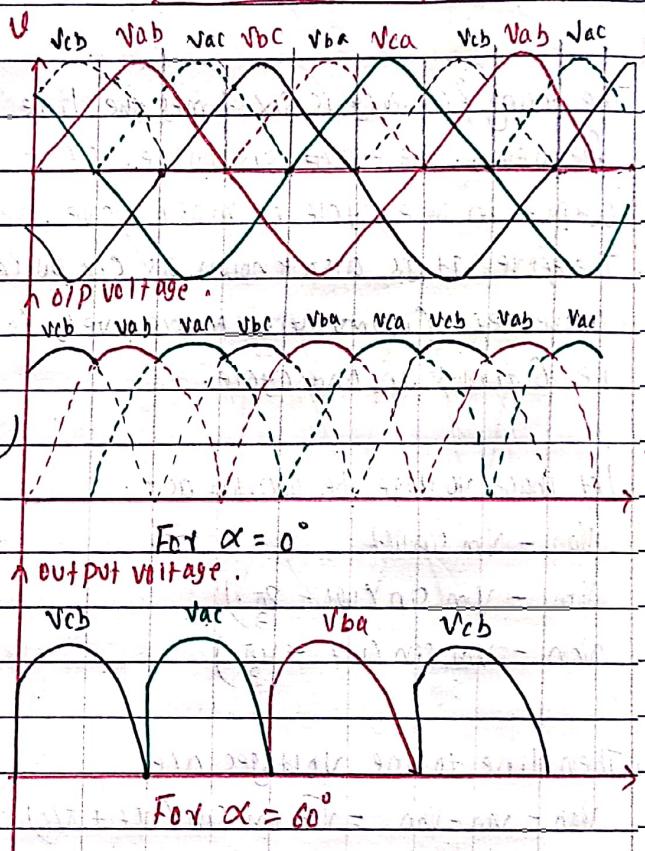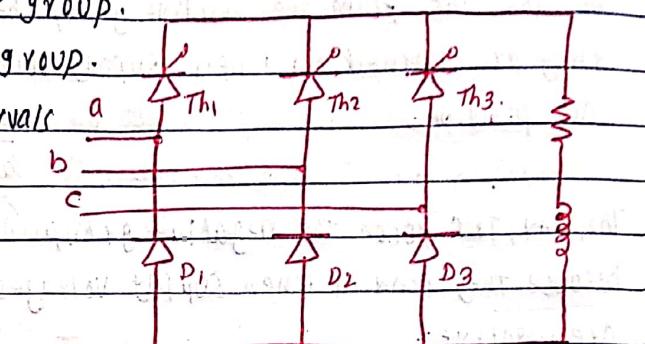
$$V_{bc} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$



\* When  $\alpha \leq \pi/3$ , the output voltage wave is continuous.

$$V_{ac} = \frac{3}{2\pi} \left[ \int_{5\pi/6+\alpha}^{\pi/2} V_{ab} d(\omega t) + \int_{\pi/2}^{7\pi/6+\alpha} V_{ac} d(\omega t) \right] = \frac{3\sqrt{3} V_m (1 + \cos \alpha)}{2\pi}$$

\* When  $\alpha > \pi/3$  the output voltage wave is discontinuous.

$$V_{ac} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi/6} V_{ac} d(\omega t) = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi/6} \sqrt{3} V_m \sin\left(\omega t - \frac{\pi}{6}\right) d(\omega t) = \frac{3\sqrt{3} V_m (1 - \cos \alpha)}{2\pi}$$


Three phase fully controlled bridge rectifier:

$\text{Th}_1, \text{Th}_3, \text{Th}_5$  form the positive group because they are turned on when supply voltages are positive.

$\text{Th}_2, \text{Th}_4, \text{Th}_6$  form the negative group because they conduct when supply voltages are negative.

The firing frequency is six times the line frequency. There are six pulses of output in one cycle of input wave.

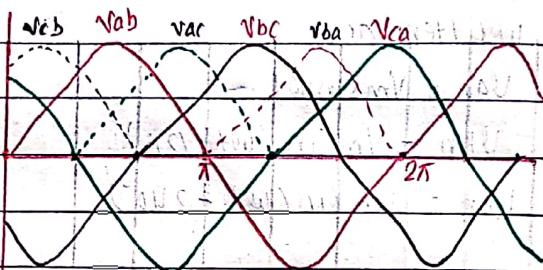Therefore, it is also known as six pulse converter. Commutation occurs every  $60^\circ$  i.e. 6 times in one cycle.



Let phase voltage be written as

$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = V_m \sin (\omega t - \frac{2\pi}{3})$$

$$V_{cn} = V_m \sin (\omega t - \frac{4\pi}{3})$$

Then line to line voltages are

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin (\omega t + \frac{\pi}{6})$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_m \sin (\omega t - \frac{\pi}{2})$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_m \sin (\omega t + \frac{5\pi}{6})$$

Average output voltage is

$$V_{dc} = \frac{1}{(2\pi)} \int_{\pi/6+\alpha}^{\pi/2+\alpha} V_{ab} d(\omega t) = \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi/2+\alpha} \sqrt{3} V_m \sin (\omega t + \frac{\pi}{6}) d(\omega t)$$

$$\therefore V_{dc} = \frac{3\sqrt{3}}{\pi} V_m \cos \alpha$$

when  $\alpha \leq 60^\circ$ , the instantaneous output voltages will have positive part only.

However, for  $\alpha > \pi/3$ , the instantaneous output voltages will have negative part also. However, the current through thyristor can flow only in forward direction. Therefore, output current will be positive only.

### Fourier Analysis:

The rectifier output voltage  $V_o(t)$  can be described by a Fourier series as.

$$V_o(t) = \frac{A_0}{2} + \sum_{n=1}^{\infty} (A_n \cos n\omega t + B_n \sin n\omega t)$$

$$\text{where, } A_0 = \frac{2}{T} \int_0^T V_o(t) dt$$

$$A_n = \frac{2}{T} \int_0^T V_o(t) \cos n\omega t dt$$

$$B_n = \frac{2}{T} \int_0^T V_o(t) \sin n\omega t dt$$

For Single phase half-wave Rectifier.


$$A_0 = \frac{2}{2\pi} \left[ \int_0^{\pi} V_m \sin \omega t dt + \int_{\pi}^{2\pi} 0 dt \right]$$

$$= \frac{2}{2\pi} V_m \int_0^{\pi} \sin \omega t dt$$

$$= \frac{V_m}{\pi} - \cos \omega t \Big|_0^{\pi}$$

$$= \frac{V_m}{\pi} (-(-1) + 1)$$

$$= \frac{2V_m}{\pi}$$

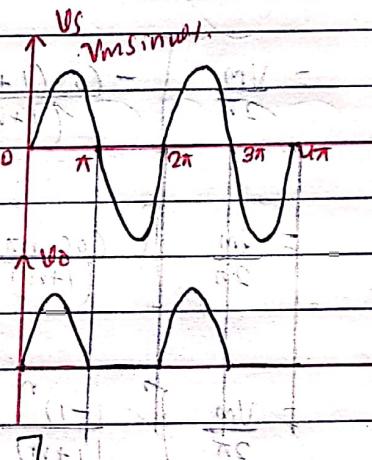

$$\begin{aligned}
 A_n &= \frac{2}{2\pi} \left[ \int_0^{2\pi} V_m \sin wt \cdot \cos nw t \, dt + \int_{2\pi}^{\infty} 0 \cdot \cos nw t \, dt \right] \\
 &= \frac{V_m}{2\pi} \int_0^{\pi} 2 \sin wt \cdot \cos nw t \, dw t \\
 &= \frac{V_m}{2\pi} \int_0^{\pi} [ \sin(1+n)wt + \sin(1-n)wt ] \, dw t \\
 &= \frac{V_m}{2\pi} \left[ -\frac{\cos(1+n)\pi}{1+n} - \frac{\cos(1-n)\pi}{1-n} \right] \\
 &= \frac{V_m}{2\pi} \left[ -\frac{\cos(1+n)\pi}{(1+n)} + \frac{1}{(1+n)} - \frac{\cos(1-n)\pi}{(1-n)} + \frac{1}{(1-n)} \right] \\
 &= \frac{V_m}{2\pi} \left[ \frac{\cos n\pi}{(1+n)} + \frac{\cos n\pi}{1-n} + \frac{1}{(1+n)} + \frac{1}{(1-n)} \right] \\
 &= \frac{V_m}{2\pi} \left[ \frac{(-1)^n}{(1+n)} + \frac{(-1)^n}{(1-n)} + \frac{1}{1+n} + \frac{1}{1-n} \right] \\
 &= \frac{V_m}{2\pi} \left[ \frac{(-1)^n(1-n) + (-1)^n(1+n)}{1-n^2} + \frac{1-n+1+n}{1-n^2} \right] \\
 &= \frac{V_m}{2\pi} \left[ \frac{2(-1)^n + 2}{1-n^2} \right] \\
 &= \frac{V_m}{2\pi} \cdot 2 \left[ \frac{1+(-1)^n}{1-n^2} \right] = \frac{V_m}{\pi} \left[ \frac{1+(-1)^n}{1-n^2} \right]
 \end{aligned}$$

For,  $n = \text{odd}$ .

$$A_n = 0$$

For  $n = \text{even}$ .

$$A_n = \frac{2V_m}{\pi} \cdot \frac{1}{(1-n^2)}$$

Similarly,

$$B_n = \frac{2}{2\pi} \left[ \int_0^{\pi} V_m \cos nt \cdot \sin nw t \, dt + \int_{\pi}^{2\pi} V_m \sin nt \cdot \cos nw t \, dt \right]$$

$$= \frac{V_m}{2\pi} \left[ \int_0^{\pi} 2 \sin nt \cdot \sin nw t \, dt \right]$$

$$= \frac{V_m}{2\pi} \left[ \int_0^{\pi} (\cos(1-n)wt - \cos(1+n)wt) \, dt \right]$$

$$= \frac{V_m}{2\pi} \left[ \left| \frac{\sin(1-n)wt}{1-n} - \frac{\sin(1+n)wt}{1+n} \right| \Big|_0^{\pi} \right]$$

$$= \frac{V_m}{2\pi} \left[ \frac{\sin(1-n)\pi}{1-n} - \frac{\sin(1+n)\pi}{1+n} \right]$$

$$= 0, \quad B_n = \frac{V_m}{2\pi} \text{ for } n=1$$

Then, Fourier series becomes.

$$v_0 = \frac{A_0}{2} + \sum_{n=1}^{\infty} (A_n \cos nt + B_n \sin nt)$$

$$= \frac{2V_m}{2\pi} + \sum_{n=2,4,6,\dots}^{\infty} \frac{2V_m}{\pi} \frac{1}{(1-n)} (\cos nt)$$


$$= \frac{V_m}{\pi} + -\frac{2V_m}{3\pi} \cos 2wt - \frac{2V_m}{15\pi} \cos 4wt - \frac{2V_m}{35\pi} \cos 6wt -$$

$$+ \frac{V_m}{2} \sin wt$$
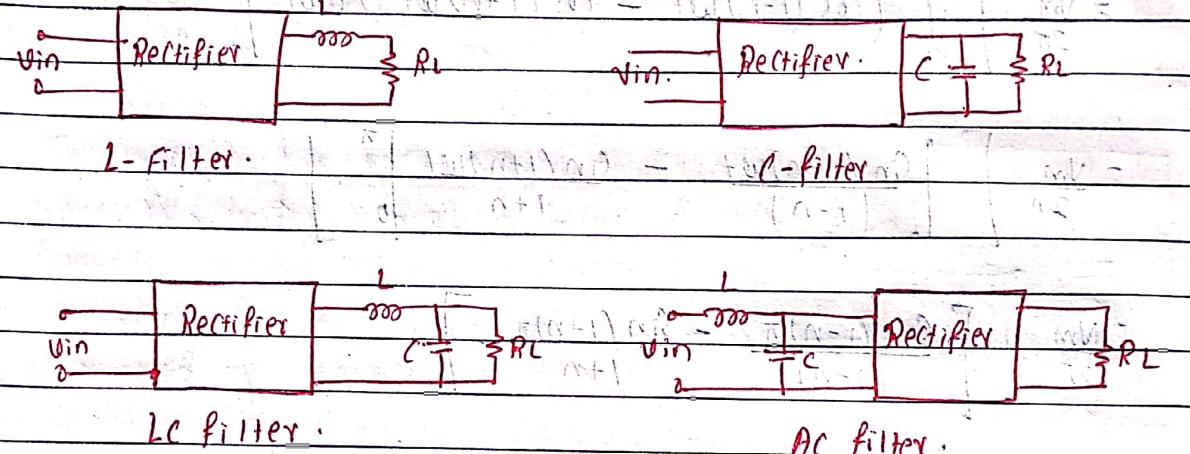
## Filtering:

The output voltage waveform of rectifiers are not pure dc, it has harmonics.

Filter can be used to smooth out the dc output voltage. The dc filters are usually L, C and LC type. Due to rectification action, the input current of rectifier also contains harmonics and ac filter is used to filter out some of the harmonics from the supply system. The ac filters are usually LC type.



## Half wave Rectifier with Capacitor Filter.

The capacitor C is charged during the conduction period to peak value of  $V_m$ .

Therefore energy is stored in the shunt

capacitor. The capacitor delivers energy

to the load during the time when

the input voltage is less than the




capacitor voltage.

The capacitor charges almost simultaneously to  $V_m$ .

$$\therefore V_c(t_1) = V_m$$

The capacitor discharges exponentially through  $R \cdot g$  is given by the equation.
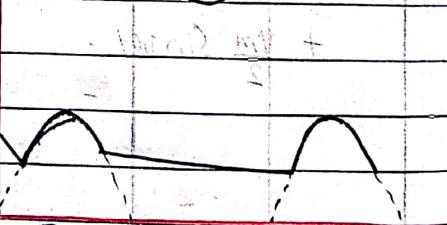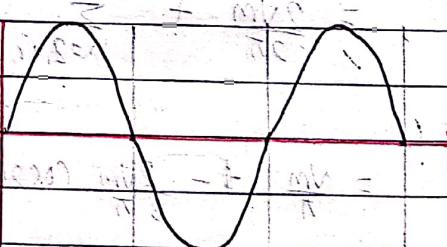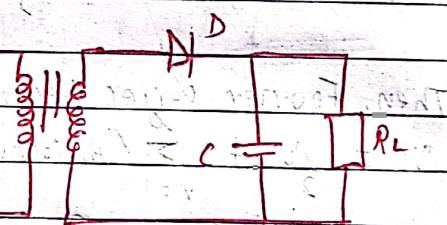
$$V_c + R_i = 0 \quad \dots \dots \dots \textcircled{1}$$



$T_1$  = Charging time  
 $T_2$  = Discharging time.

$$i = \frac{dq}{dt} = \frac{d(CV_c)}{dt} = C \frac{dV_c}{dt}$$

From equation ①

$$V_c + R C \frac{dV_c}{dt} = 0$$

$$\text{or, } V_c = -RC \frac{dV_c}{dt}$$

$$\text{or, } \frac{dt}{RC} = -\frac{dV_c}{V_c}$$

$$\text{or, } \int \frac{dV_c}{V_c} = -\frac{1}{RC} \int dt$$

$$\text{or, } \ln V_c = -t + K \quad \text{--- eqn ②}$$

$$\text{At, } t=0, V_c = V_m$$

$$\text{Then, } K = \ln V_m$$

$$\text{Now, } \ln V_c = -t + \ln V_m.$$

$$\text{or, } \ln \left( \frac{V_c}{V_m} \right) = -\frac{t}{RC}$$

$$\text{or, } V_c = V_m e^{-t/RC}$$

$$\text{Peak to peak ripple voltage } V_{r(P-P)} = V_0(t_1) - V_0(t_2)$$

$$= V_m - V_m e^{-t_2/RC}$$

$$= V_m (1 - e^{-t_2/RC})$$

$$= V_m [1 - (1 - \frac{t_2}{RC})]$$

$$\therefore e^m = 1 - m + \frac{m^2}{2!} + \dots$$

\ Neglecting .

$$\therefore V_{r(P-P)} = \frac{V_m}{RC} \cdot t_2 = \frac{V_m}{fRC} \quad t_1 + t_2 \approx t_2 = T = \frac{1}{f} \quad t_1 < t_2$$

$$V_{dc} = V_m - \frac{V_{r(P-P)}}{2} = V_m - \frac{V_m}{2fRC} = V_m \left( 1 - \frac{1}{2fRC} \right)$$

The rms value of ripple voltage  $V_r = \frac{V_r}{\sqrt{3}} = \frac{V_m}{2fRC \times \sqrt{2}}$ .


$$\therefore \text{Ripple factor} = \frac{V_r}{V_{dc}} = \frac{V_m}{2V_{dc}fRC} \times \frac{2fRC}{V_m(2fRC-1)}$$

$$= \frac{1}{\sqrt{2}(2fRC-1)}$$

i.e., RF is independent on the input voltage.

Full wave Rectifier with capacitor filter.

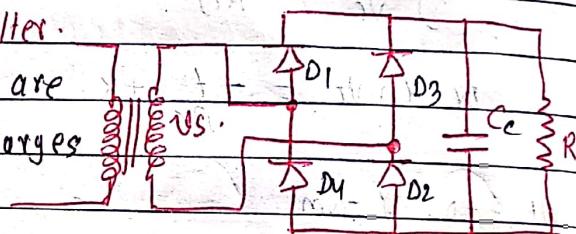
When,  $V_s < V_c \Rightarrow D_1, D_3$ , or  $D_2, D_4$  are reversed biased and capacitor  $C_c$  discharges through the load resistance  $R$ .



$t_1 \rightarrow$  charging time.

$t_2 \rightarrow$  discharging time.

$$\text{At } t = t_1, V_c(t) = V_m.$$

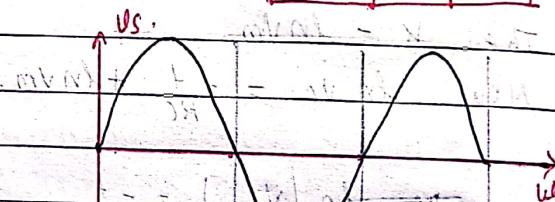

The capacitor discharges exponentially through  $R$ .

$$\frac{1}{C_c} \int i_C dt + V_c(t=0) + R_{io}t = 0 = 10^{-3} \text{ A.s}$$

which with an initial condition of

$V_c(t=0) = V_m$  gives the discharging current as,

$$i_C = \frac{V_m}{R} = e^{-t/RC}$$

$$V_o(t) = R_{io} = V_m e^{-t/RC}.$$

Peak to peak ripple voltage,  $V_r(p-p) = V_o(t=t_1) - V_o(t=t_2)$

$$= V_m - V_m e^{-t_2/RC}$$

$$= V_m (1 - e^{-t_2/RC})$$

Since,  $e^n = 1 - n$ .

$$V_{(P-P)} = V_m \left( 1 - \left( 1 - \frac{t_2}{RC} \right) \right) = V_m \frac{t_2}{RC} \quad t_2 \approx T = \frac{1}{2f}$$

$$= \frac{V_m}{2fRC}$$

Average load voltage  $V_{dc}$  is

$$V_{dc} = \frac{v_m - V_{(P-P)}}{2} = \frac{v_m - V_m}{2fRC}$$

The rms output & ripple voltage  $V_{ac}$  can be found as,

$$V_{ac} = \frac{V_{(P-P)}}{2\sqrt{2}} = \frac{V_m}{2\sqrt{2}fRC}$$

$$\therefore \text{Ripple factor} = \frac{V_{ac}}{V_{dc}} = \frac{\frac{V_m}{2\sqrt{2}fRC}}{\frac{V_m}{2fRC} \times (1 - \frac{1}{2\sqrt{2}})} = \frac{1}{\sqrt{2}(1 - \frac{1}{2\sqrt{2}})}$$

### Power factor improvement


The input current  $I_s$  lags the input voltage  $V_s$  in the rectifier circuit. When the firing angle is increased,  $I_s$  lags by larger angle with  $V_s$  and input power factor becomes poor.

#### ① Extinction Angle control method:

In this method, the average value of output voltage of rectifier is controlled by varying the extinction angle ( $\beta$ ) rather than the changing firing angle ( $\alpha$ ). The extinction angle ( $\beta$ ) is the angle at which the conduction is forcefully extinguished before the natural zero end of positive half cycle. The angle  $\beta$  is measured back from the zero end of the positive half cycle.

The Switches  $S_1, S_2, S_3$  and  $S_4$  are GTO

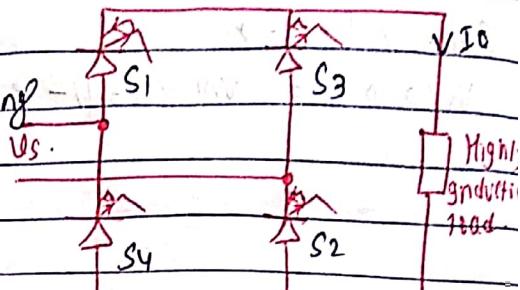Switches which can be turned on by applying positive gate signal and turned off by applying negative gate signals.




During the half cycle of input voltage,  $S_1$  &  $S_2$

are turned on simultaneously at  $\omega t = 0$  and

at  $\omega t = \pi - \beta$ ,  $S_2$  is turned off and at

the same time  $S_4$  is turned on.

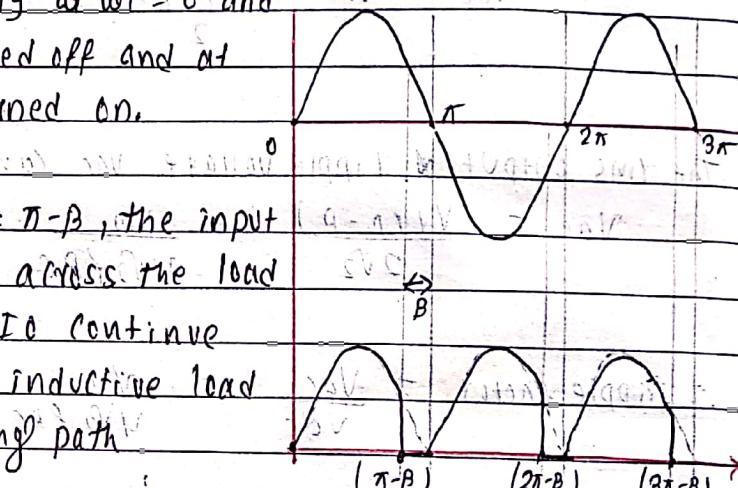When  $S_2$  turns off at  $\omega t = \pi - \beta$ , the input voltage  $V_s$  doesn't appear across the load but the output current  $I_o$  continues to flow due to highly inductive load through the free-wheeling path  $S_1$ -load- $S_4$ .



At  $\omega t = \pi$ ,  $S_1$  is turned off and  $S_3$  is turned on so that ~~negative~~ negative half of the input voltage get rectified and appears as positive output voltage across the load.  $S_3$  is turned off and  $S_2$  is turned on at  $\omega t = 2\pi - \beta$ .

The average value of output voltage can be changed by varying extinction angle  $\beta$ .

Average value of o/p voltage is  $V_{dc} = \frac{1}{\pi} \int_0^{\pi-\beta} V_m \sin \omega t \, d\omega t$

$$= V_m \beta / \pi$$

Rms value of o/p voltage is  $V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi-\beta} (V_m \sin \omega t)^2 \, d\omega t}$

$$= \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} [(\pi - \beta) + \sin 2\beta]}$$


### Fourier Analysis.

$$A_0 = \frac{2}{\pi} \int_0^{\pi - \beta} V_m \sin \omega t \cdot d\omega t = \frac{2V_m}{\pi} [1 + \cos \beta]$$

$$A_n = \frac{2}{\pi} \int_0^{\pi - \beta} V_m \sin \omega t \cos n \omega t \cdot d\omega t .$$

$$B_n = \frac{2}{\pi} \int_0^{\pi - \beta} V_m \sin \omega t \cdot \sin n \omega t \cdot d\omega t .$$

### ① Symmetrical Angle control method.

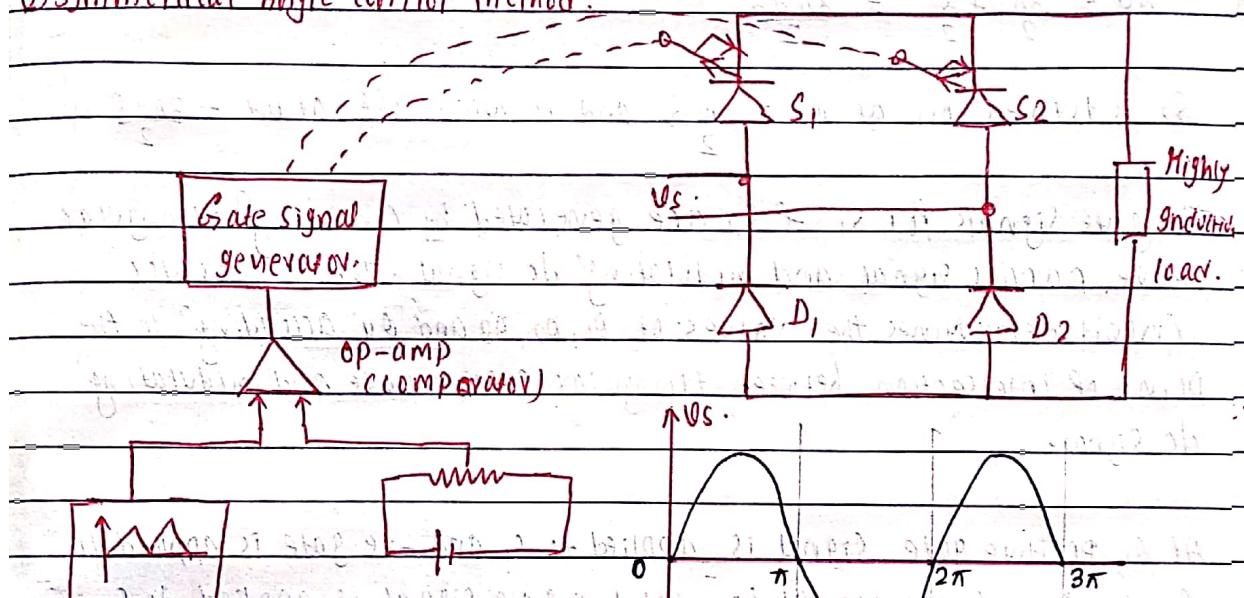


### Triangular wave generator.

In this method, the magnitude of output voltage is controlled by firing as well as extinction angle control.

During +ve half cycle of input

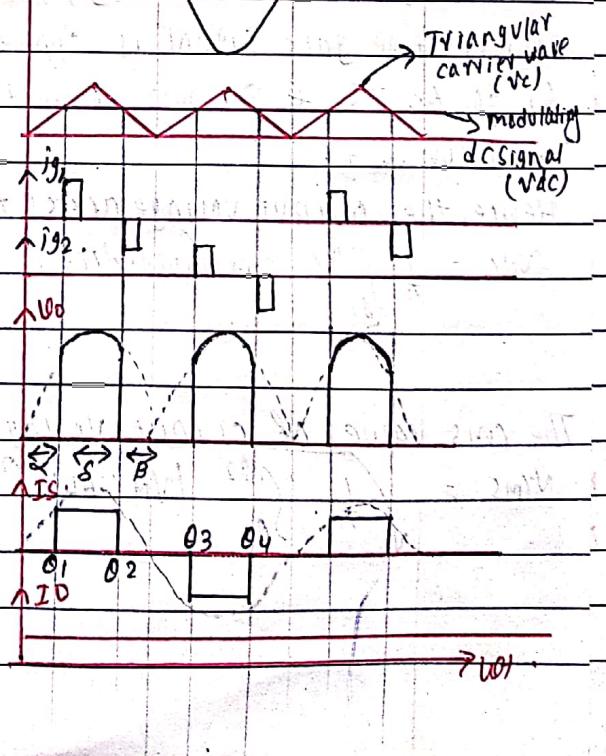voltage  $V_{AS}$ ,  $S_1 \& D_2$  are forward biased and  $S_2 \& D_1$  are reverse biased. The switch  $S_1$  is turned on at  $\omega t = \frac{\pi - \delta}{2} + 0 \frac{\pi + \delta}{2}$



Similarly during -ve half cycle of input voltage  $V_s$ ,  $S_2$  &  $D_1$  are forward biased and  $S_1$  &  $D_2$  are reversed biased.

$$\theta_1 = \frac{\pi}{2} - \frac{\delta}{2} = \frac{\pi - \delta}{2}$$

$$\theta_2 = \frac{\pi}{2} + \frac{\delta}{2} = \frac{\pi + \delta}{2}$$

$$\theta_3 = \frac{3\pi}{2} - \frac{\delta}{2} = \frac{3\pi - \delta}{2}$$

$$\theta_4 = \frac{3\pi}{2} + \frac{\delta}{2} = \frac{3\pi + \delta}{2}$$

$S_2$  is turned on at  $\omega t = \frac{3\pi - \delta}{2}$  and is turned off at  $\omega t = \frac{3\pi + \delta}{2}$ .

The gate signals for  $S_1$  &  $S_2$  are generated by comparing triangular wave carrier signal and modulating dc signal. The comparator circuit determines the values of  $\theta_1, \theta_2, \theta_3$  and  $\theta_4$  according to the point of intersection between triangular carrier wave and modulating dc signal.

At  $\theta_1$ , positive gate signal is applied to  $S_1$  and -ve gate is applied to  $S_1$  at  $\theta_2$ . Similarly at  $\theta_3$ , positive gate signal is applied to  $S_2$  and negative gate signal is applied to  $S_2$  at  $\theta_4$ . Therefore, from  $\theta_1$  to  $\theta_2$ ,  $S_1$  &  $D_2$  will conduct and from  $\theta_3$  to  $\theta_4$ ,  $S_2$  &  $D_1$  will conduct.

Hence, the output voltage across the load is

$$V_{DC} = \frac{1}{\pi} \int_{\theta_1}^{\theta_2} V_m \sin \omega t \cdot d\omega t = \frac{2V_m}{\pi} \sin \frac{\delta}{2}$$

The rms value of output voltage is

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\theta_1}^{\theta_2} (V_m \sin \omega t)^2 d\omega t} = \frac{V_m}{\sqrt{2}} \sqrt{8 + \sin \delta}$$